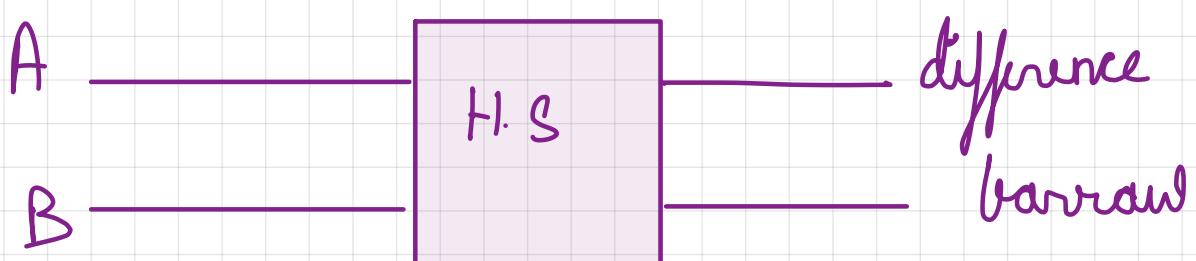


ADITYA KUNDU

Half Subtractor :-

- ① It is a combinational circuit
 - ② It performs the arithmetic subtraction of two binary digits
 - ③ It produces two outputs ① difference and ② borrow.

Block diagram :-




Truth Table :-

A	B	diff	borrow	minterm
0	0	0	0	$\bar{A}\bar{B}$
0	1	1	1	$\bar{A}B$
1	0	1	0	$A\bar{B}$
1	1	0	0	AB

$$\text{difference} = (\bar{A}B) + (A\bar{B}) \quad \xrightarrow{\text{from truth table}} \quad \overline{A \oplus B}$$

$$\text{barrow} = \bar{A}B$$


Circuit diagram :-

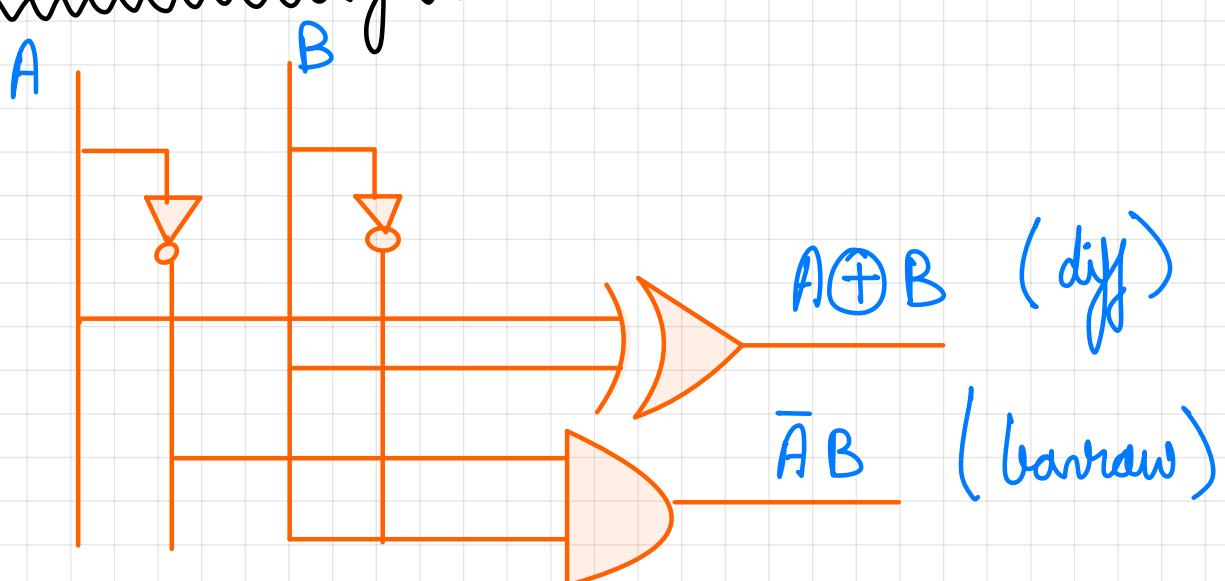

■ Full Subtractor :-

- (i) It is a combinational circuit.
- (ii) It performs arithmetic subtraction of three binary digits.
- (iii) It also produces two outputs (i) difference and (ii) borrow.

■ Block diagram :-

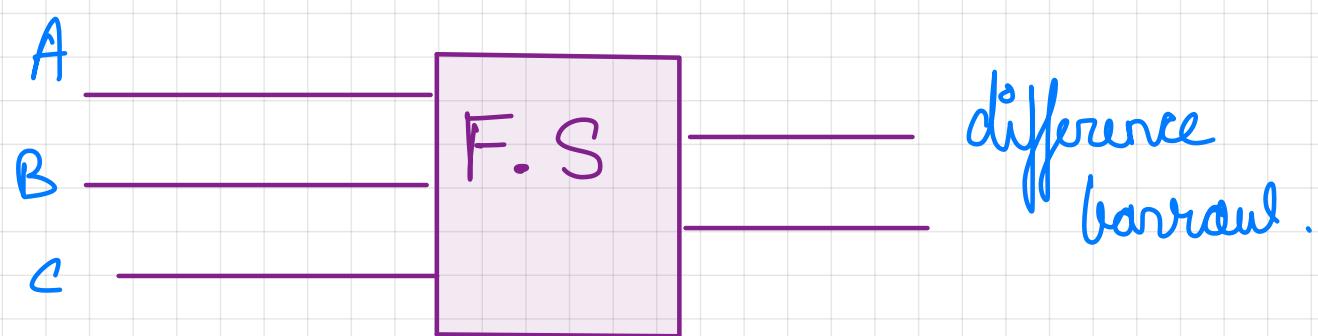

■ Truth Table :-

A	B	C	diff	borrow	minterm
0	0	0	0	0	$\bar{A}\bar{B}\bar{C}$
0	0	1	1	1	$\bar{A}\bar{B}C$
0	1	0	1	1	$\bar{A}B\bar{C}$
0	1	1	0	1	$\bar{A}BC$
1	0	0	1	0	$A\bar{B}\bar{C}$
1	0	1	0	0	$A\bar{B}C$
1	1	0	0	0	$AB\bar{C}$
1	1	1	1	1	ABC

$$\text{difference} = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + ABC$$


$$= [\bar{A}(\bar{B}C + B\bar{C})] + [A(\bar{B}\bar{C} + BC)]$$

$$= [\bar{A}(B \oplus C)] + [A(B \oplus C)]$$

$$= A \oplus B \oplus C$$


$$\begin{aligned}
 \text{borrow} &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + ABC \\
 &= \bar{A}(\bar{B}C + B\bar{C}) + BC(\bar{A} + A) \quad [\because \bar{A} + A = 1] \\
 &= \bar{A}(B \oplus C) + BC
 \end{aligned}$$

Circuit diagram :-

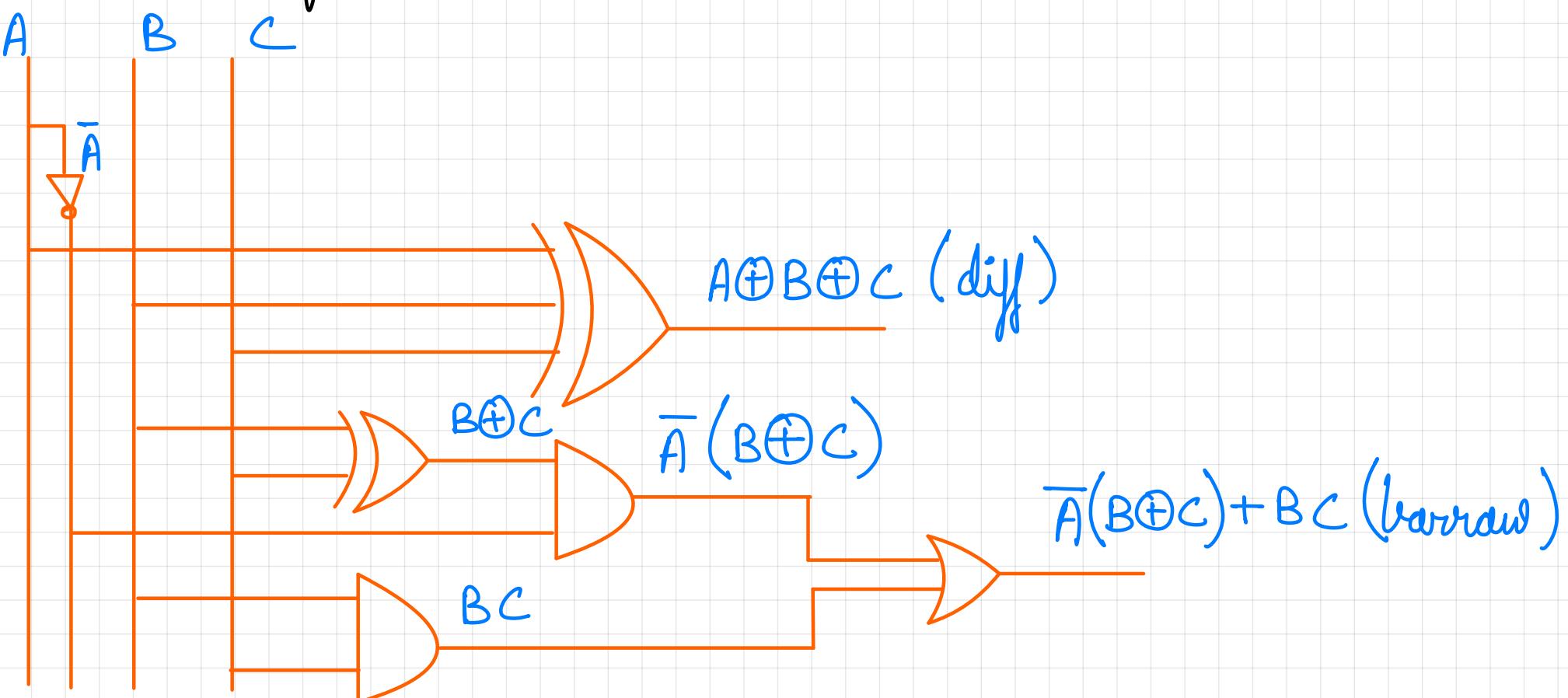


Full Adder Using Half Adder :-


Block diagram :-

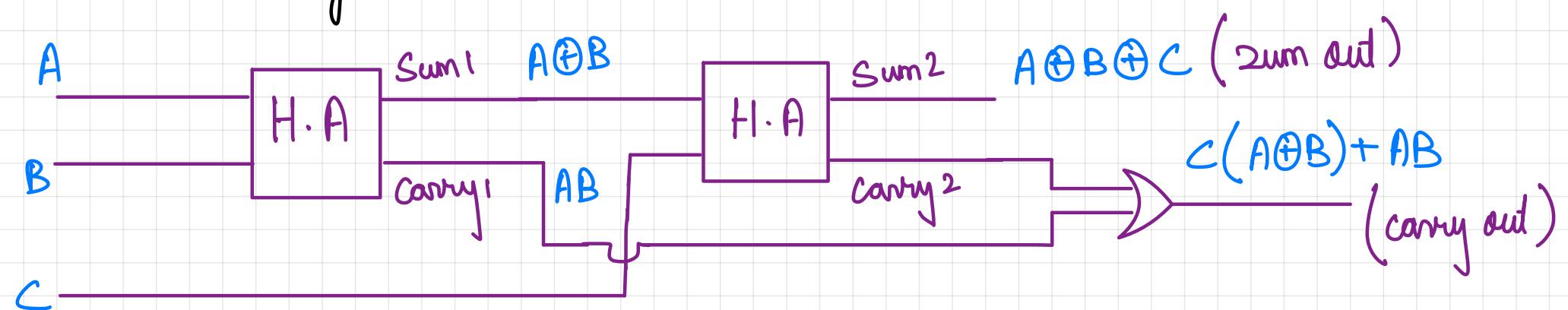

Circuit diagram :-

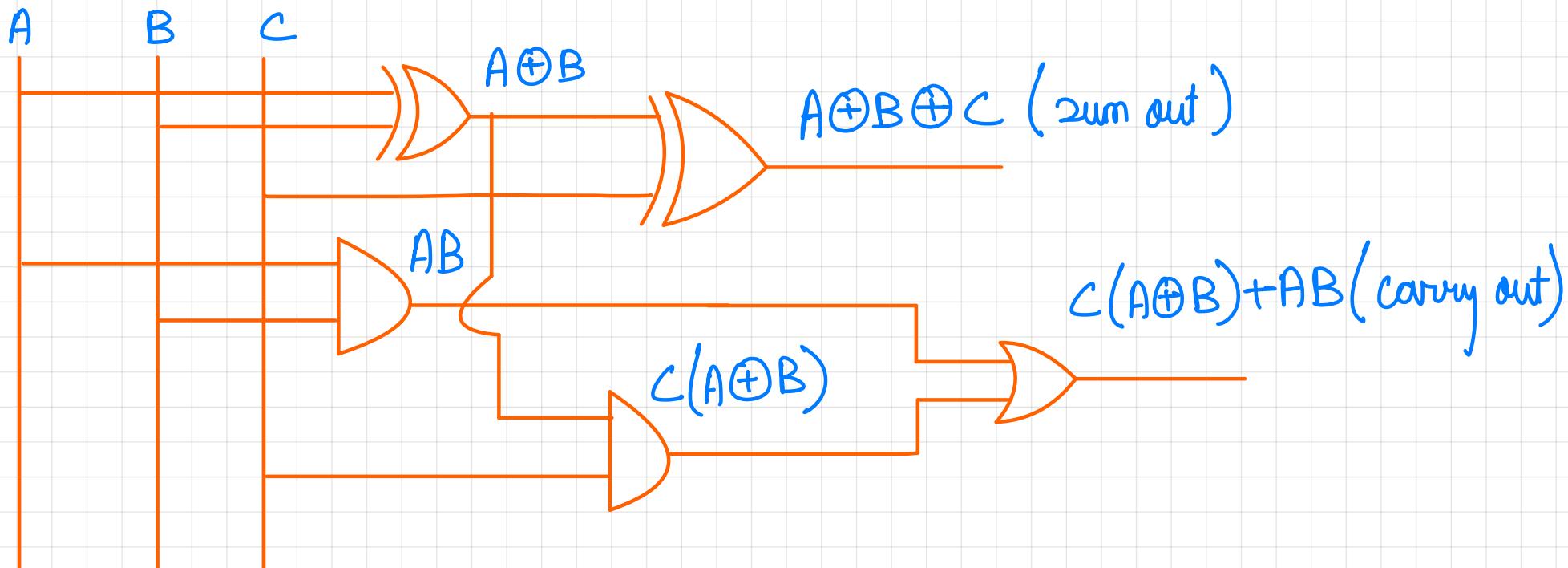

Logic diagram Using Basic gates :-

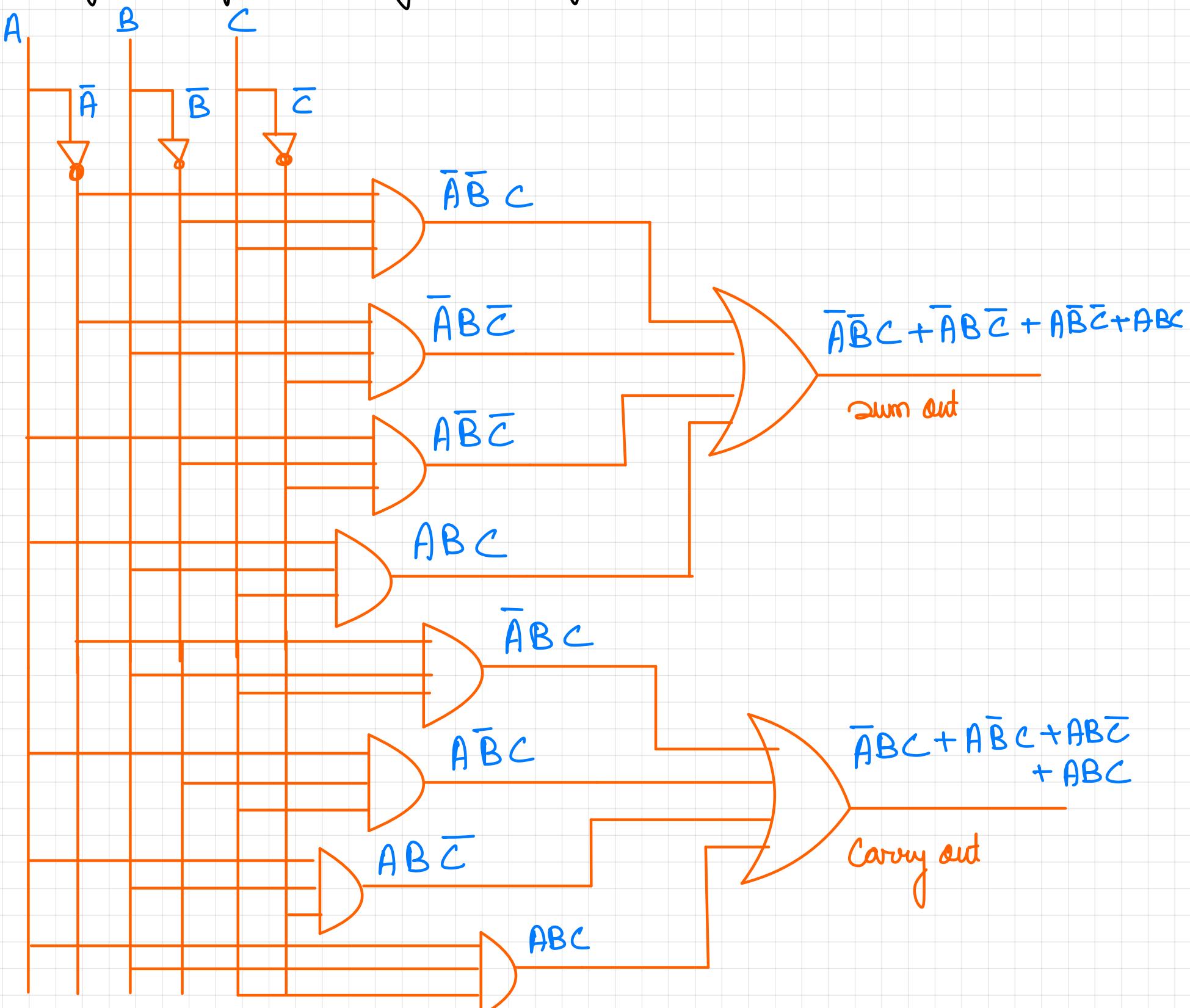

Karnaugh Map (K-Map)

15/Sep/2022

The Karnaugh map technique provide a systematic method for simplifying and manipulating switching expressions. In this technique the information contained in a truth table or available in the POS form or SOP form is represented on the K-Map.

$$Y = \sum_m (0, 3)$$



$$\text{Step 1: } 2^n = 3 \leq 4 \\ n = 2$$

Variable values in K-Map follow gray code only! Not Binary

Step-2:

		0	1
		0	1
A	B	0	1
0	0	1	0
1	0	0	1
		2	3

group 1 → $\bar{A}\bar{B}$

group 2 → AB

A	B	
0	0	0
0	1	1
1	0	2
1	1	3

Step-3: Group Making

① The groups will be made with max no. of 1s (SOP), 0s (POS)

Remember

② The total no of 1s within the group must be the power of 2.

Step-4:

		A	B	
		0	0	$\bar{A}\bar{B}$
		0	1	AB
Y = $\bar{A}\bar{B} + AB$				

Q. $Y = \sum m(2, 3, 4, 5)$

Step-4

A B C

group 1 → 0 1 1 → $\bar{A}B$

group 2 → 1 0 0 → $A\bar{B}$

$$Y = \bar{A}B + A\bar{B}$$

Don't take the changing values, take the fixed values only.

Remember

Step-3: Grouping.

		BC	00	01	11	10				
		A	0	000	1	001	3	011	2	010
		0	0	0	1	0	1	0	1	0
4	5	0	000	1	001	3	011	2	010	1
		1	000	1	001	3	011	2	010	0

$$Q.1. Y = \sum_m (0, 2, 3)$$

$$Q.2. Y = \sum_m (0, 1, 4, 5, 7)$$

Multiplexer :-

16/Sep/2022


→ It is a combinational circuit.

→ It selects one digital information from several source and transmits the selective information on a single output line.

(Many to One) → Multiple input source and one output source.

• **2x1 MUX :-**

Block diagram :-

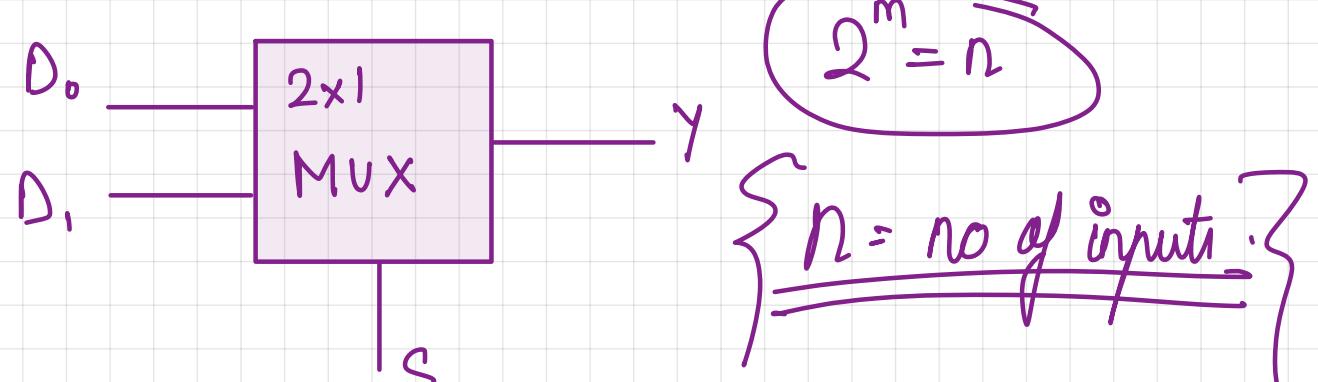


Truth Table

S	Y
0	D_0
1	D_1

$$Y = D_0 \bar{S} + D_1 S$$

Circuit diagram :-

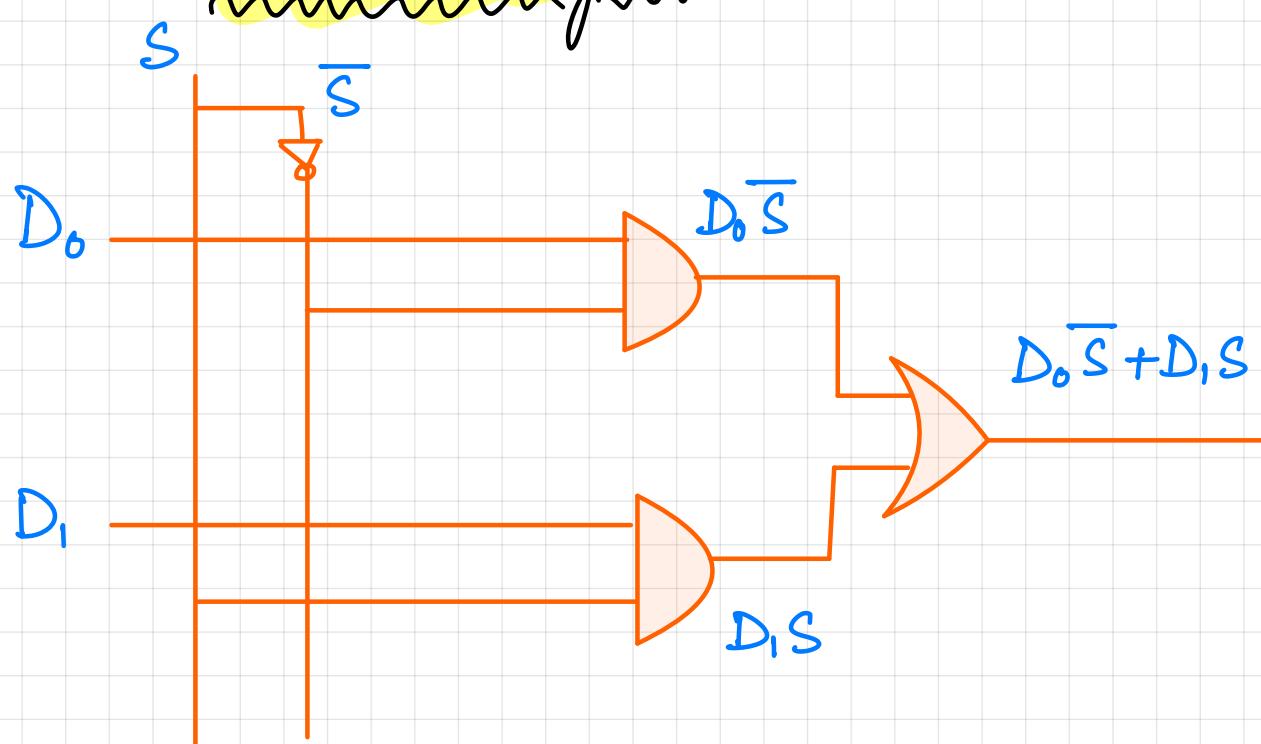

16/Sep/2022


• 8x1 MUX :-

$$2^m = n$$

$$\Rightarrow 2^m = 8$$

$$\Rightarrow m = 3$$

Block diagram

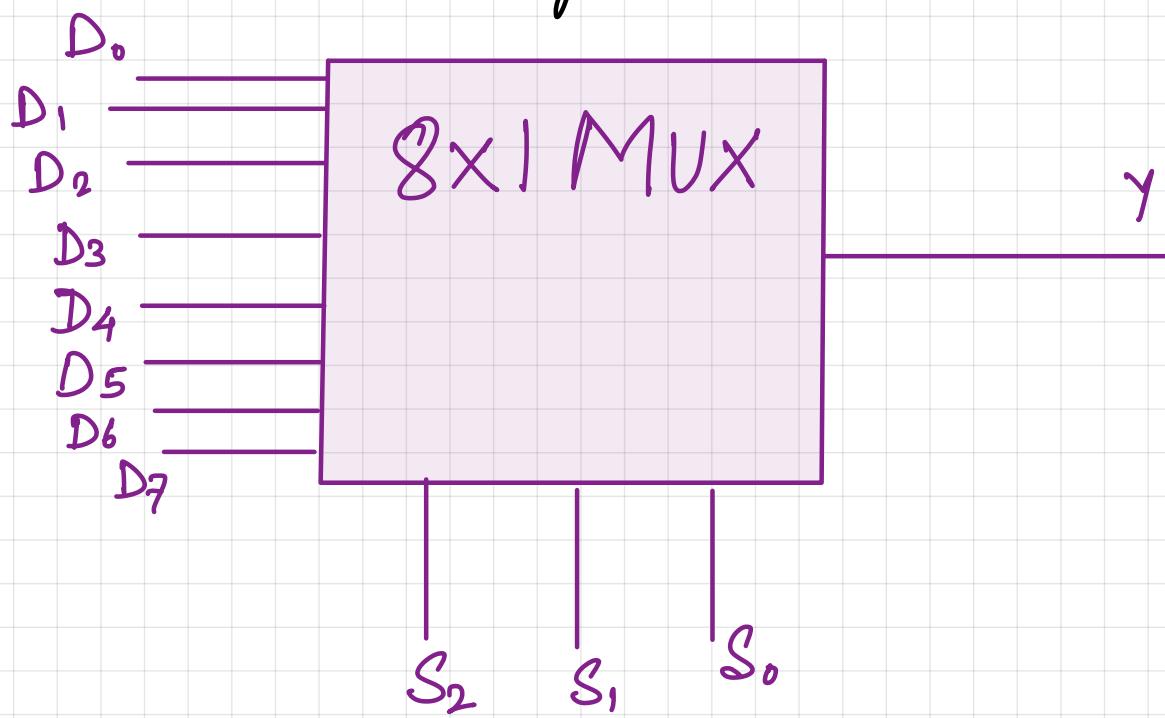


• Truth Table

S ₀	S ₁	S ₂	Y
0	0	0	D ₀
0	0	1	D ₁
0	1	0	D ₂
0	1	1	D ₃
1	0	0	D ₄
1	0	1	D ₅
1	1	0	D ₆
1	1	1	D ₇

• Logical expression

$$Y = D_0 \bar{S}_0 \bar{S}_1 \bar{S}_2 + D_1 \bar{S}_0 \bar{S}_1 S_2 + D_2 \bar{S}_0 S_1 \bar{S}_2 + D_3 \bar{S}_0 S_1 S_2 + D_4 S_0 \bar{S}_1 \bar{S}_2 + D_5 S_0 \bar{S}_1 S_2 + D_6 S_0 S_1 \bar{S}_2 + D_7 S_0 S_1 S_2$$

• Circuit diagram :-

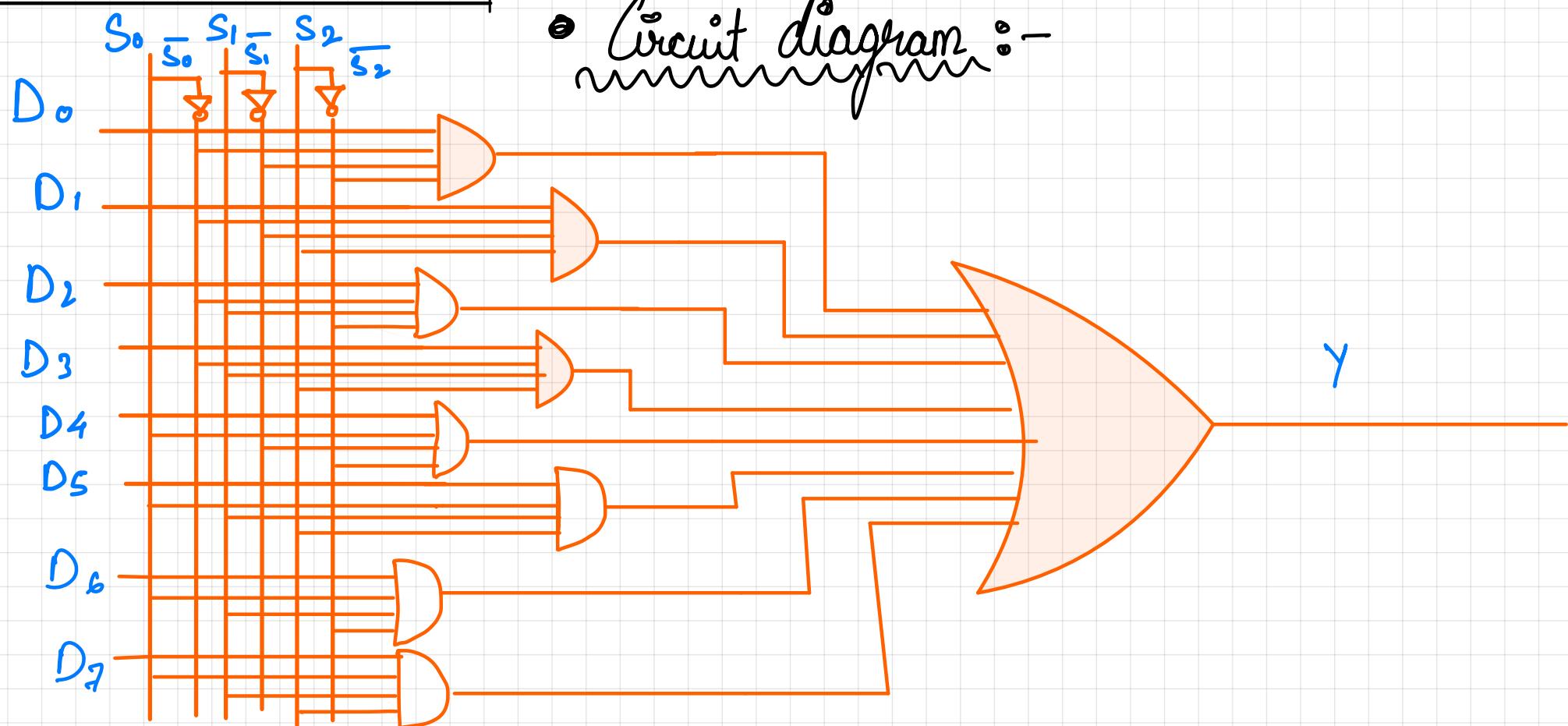


$$Q. Y = \sum_m (0, 2, 3)$$

Soln: Step-①: $2^n = 3 \simeq 4$

$$n = 2$$

Step-②:

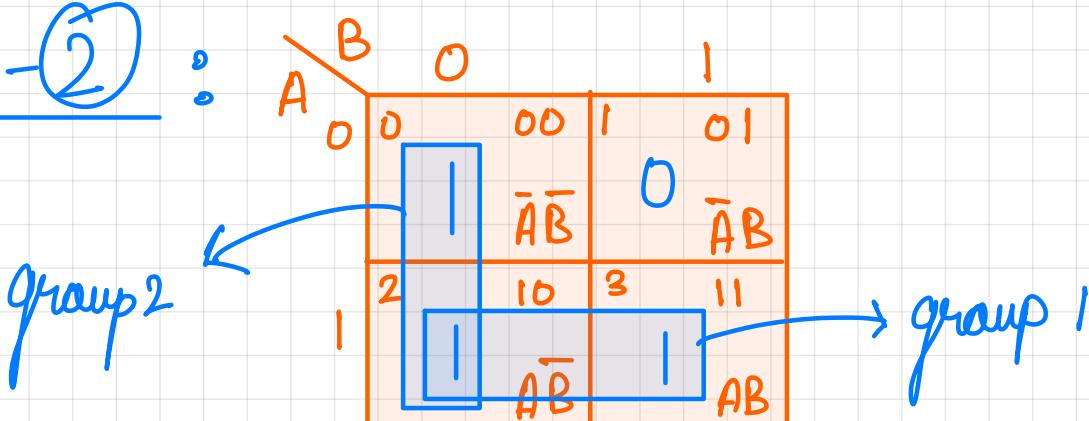

Step-③: Grouping done in K-Map.

Step-④:

A	B
1	0
0	1

group 1 → $\rightarrow A$ $\therefore Y = A + \bar{B}$


group 2 → $\rightarrow \bar{B}$

$$Q. Y = \sum_m (0, 1, 4, 5, 7)$$

Soln: Step-①: $2^n = 7 \simeq 8$

$$n = 3$$

Step-②:

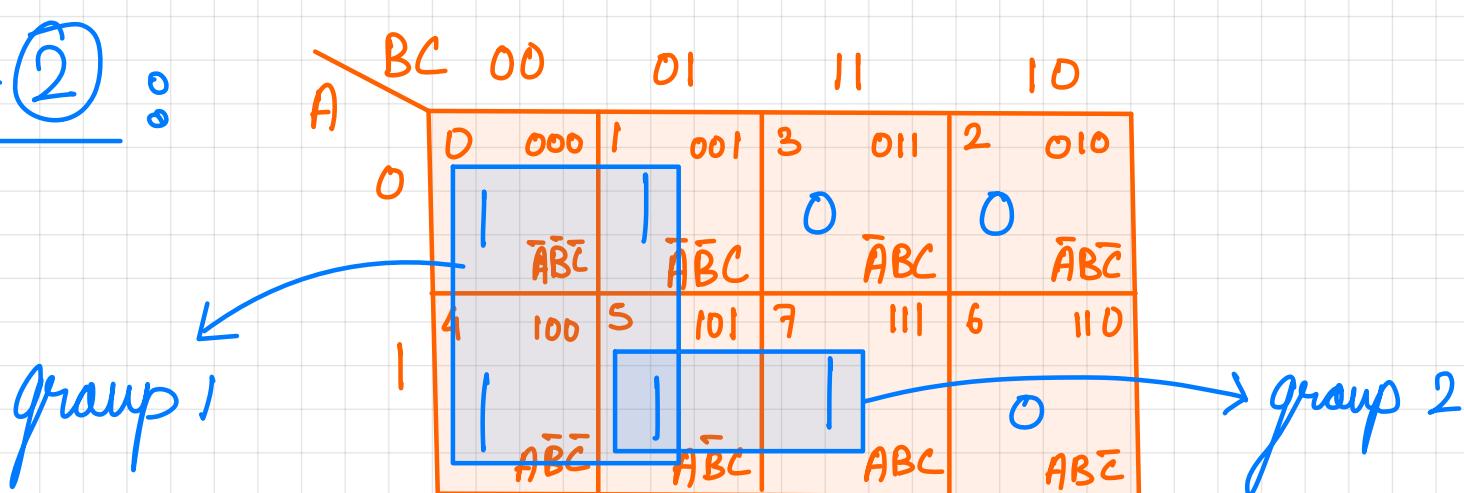

Step-③: Grouping done in K-Map

Step-④:


A	B	C
0	0	0
1	0	1

group 1 → $\rightarrow \bar{B}$ $\therefore Y = \bar{B} + AC$

group 2 → $\rightarrow AC$

$$Q. Y = \sum m(0, 1, 5, 7, 9, 13, 15)$$

Soln: Step-①: $2^n = 15 \simeq 16$

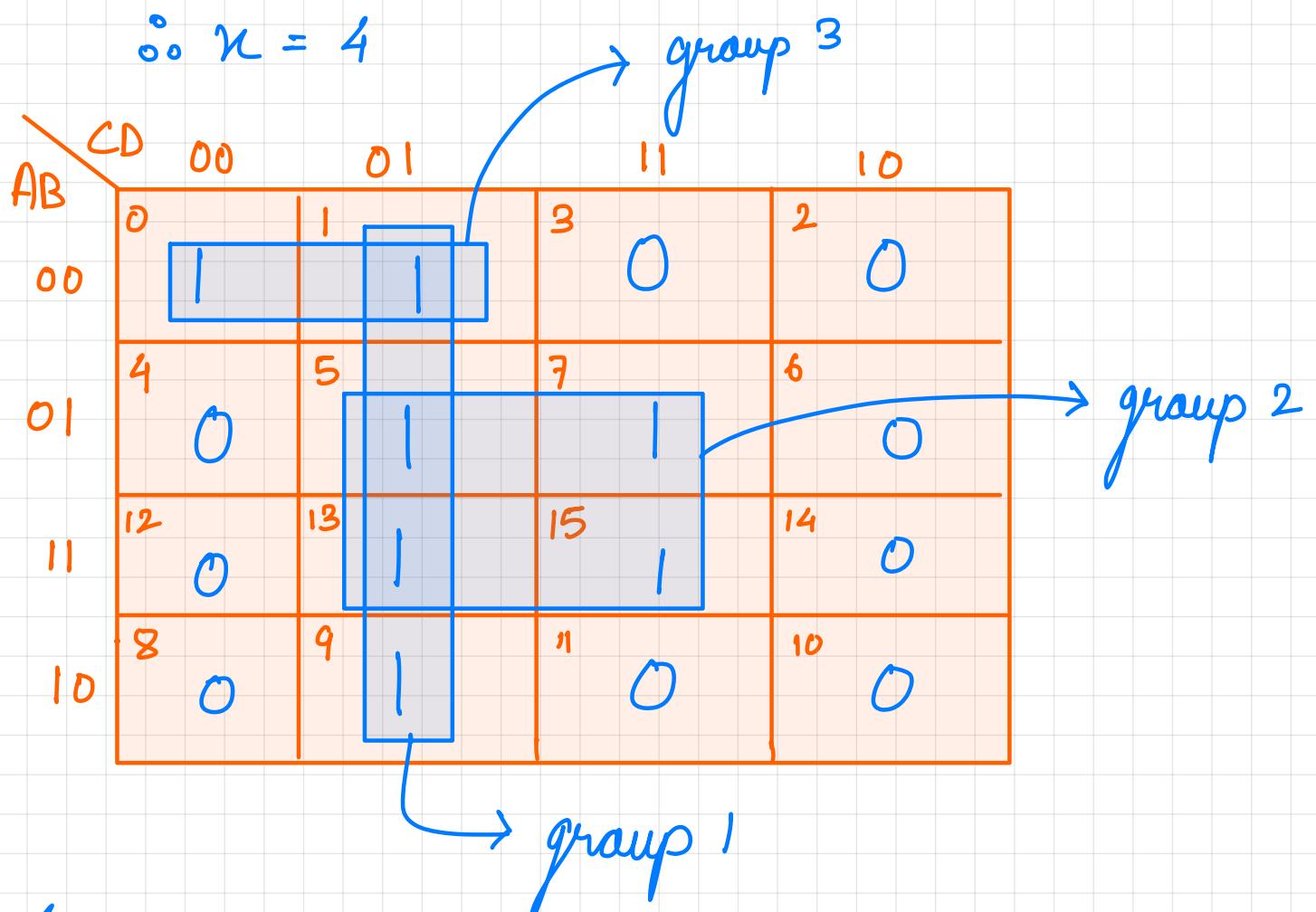

Step-②:

Step-③: Grouping as done in diagram.

Step-④:

	A	B	C	D
Group 1 →	0	0	0	1
	0	1	0	1
	1	0	0	0
Group 2 →	0	1	0	1
	0	1	1	0
	1	0	0	1
Group 3 →	0	0	0	0
	0	0	0	1

$$\therefore Y = \overline{C}D + BD + \overline{A}\overline{B}\overline{C} \quad \text{Ans}$$

$$Q. Y = \sum m(0, 2, 8, 10)$$

Soln: Step-①: $2^n = 10 \simeq 16$

$$\therefore n = 4$$

Step-②:

		CD	00	01	11	10
		A B	00	0	3	2
		00	1	0	0	1
		01	4	5	7	6
		11	12	13	15	14
		10	8	9	11	10
			1	0	0	1

Step-③: Corner grouping in K-Map. (of 4 elements)

Step-④:

A	B	C	D
0	0	0	0
0	0	1	0
1	0	0	0
1	0	1	0

group 1 → $\bar{B}\bar{D}$

$\therefore Y = \bar{B}\bar{D}$

TO DO

Q.1 $Y = \sum_m(1, 2, 5, 7, 9, 13, 15)$


Q.2 $Y = \sum_m(1, 3, 5, 7, 9, 11, 13)$

Q.3 $Y = \sum_m(1, 3, 5, 7, 9, 11, 13, 15)$

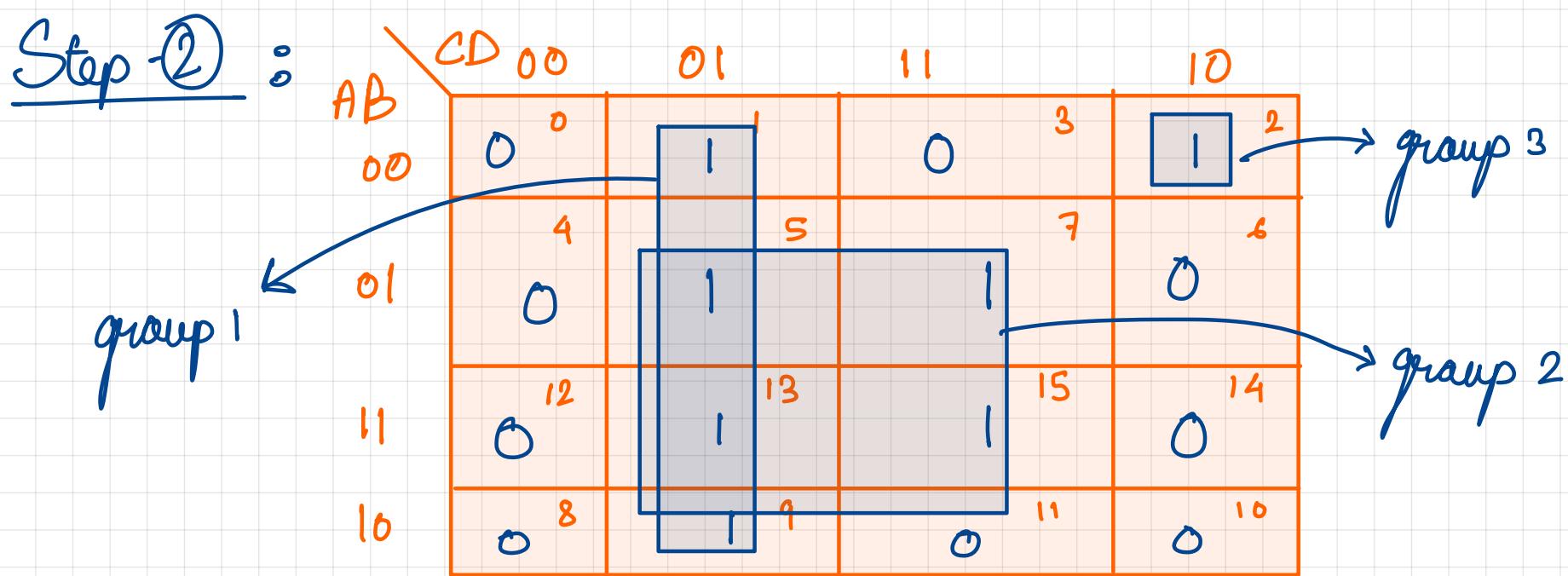Q.4 $Y = \sum_m(0, 1, 2, 3, 4, 5, 8, 9, 10, 11)$

K-Mapping

Soh ① Step ① $2^n = 15 \simeq 16$
 $\therefore n = 4$



Step-③ : Grouping in K Map.

Step-④:

A	B	C	D
0	0	0	1
0	1	0	1
1	1	0	1
1	0	0	1

A	B	C	D
0	1	0	1
0	1	1	1
1	1	0	1
1	1	1	1


A	B	C	D
0	0	1	0
0	0	0	1
1	1	1	0
1	1	1	1

$$\therefore Y = \bar{C}D + BD + \bar{A}\bar{B}C\bar{D}$$

Ans

(2) Step-① : $2^k = 13 \approx 16$

$$n = 4$$

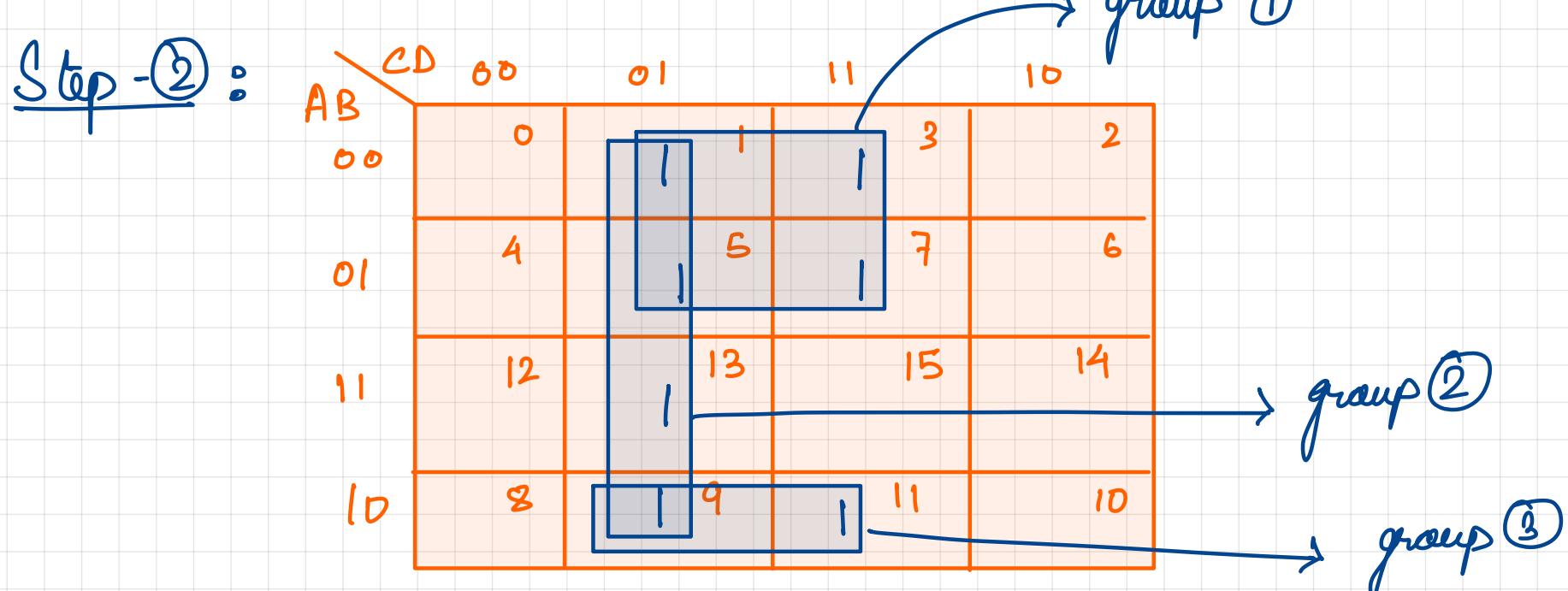

Step-③ : Grouping in K-Map.

Step - ④

A	B	C	D
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1

group ① \rightarrow $\bar{A}D \rightarrow \bar{A}D$

A	B	C	D
0	0	0	1
0	0	1	1
1	1	0	1
1	0	0	1

group ② \rightarrow $\bar{C}D \rightarrow \bar{C}D$


A	B	C	D
1	0	0	1
1	0	1	1

group ③ \rightarrow $A\bar{B}D \rightarrow A\bar{B}D$

$\therefore Y = \bar{A}D + \bar{C}D + A\bar{B}D$ Ans

③

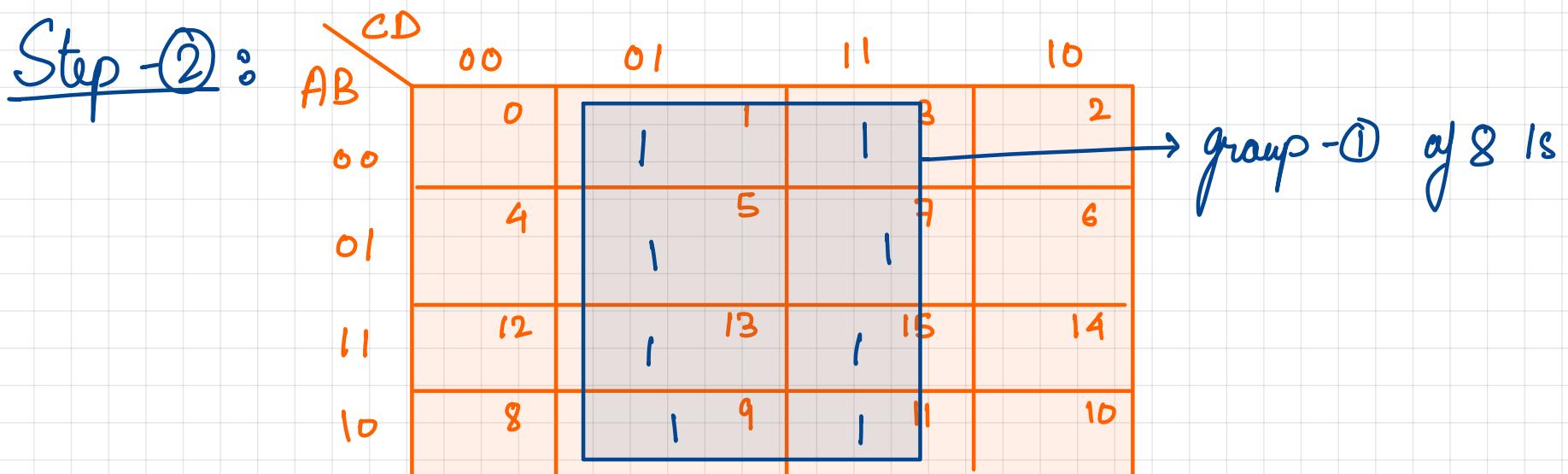Step - ① : $2^n = 15 \approx 16$
 $n = 4$



Step - ③ : Grouping on K-Map

Step - ④ :

A	B	C	D
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	1	0	1
1	1	1	1
1	0	0	1
0	0	1	1

$\therefore Y = D$

④

Step -① : $2^n = 16 \simeq 16$

$$\chi = 4$$

Step -② :

	CD 00	01	11	10
AB 00	1 0	1 1	1 3	1 2
01	1 4	1 5	1 7	1 6
11	1 2	1 3	1 5	1 4
10	1 8	1 9	1 11	1 10

group ②

group ①

Step -③ : Grouping on K-Map.

Step -④ :

group ① →

A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	1
0	0	1	0
1	0	0	0
1	0	0	1
1	0	1	1
1	0	1	0

$$\rightarrow \bar{B}$$

$$\therefore Y = \bar{A}\bar{C} + \bar{B}$$

group ② →

A	B	C	D
0	0	0	0
0	0	0	1
0	1	0	0
0	1	0	1

$$\rightarrow \bar{A}\bar{C}$$

$$\text{Q. } Y = \sum_m (0, 1, 2, 4, 5, 6, 7, 8)$$

Step -③ : Grouping

Soln: Step -① : $2^n = 16 \simeq 16$
 $\therefore \chi = 4$

Step -② :

	CD 00	01	11	10
AB 00	1	1	3	2
01	1	1	1	1
11	1	3	1	1
10	1	8	9	11

group 3

Step -④ :

A	B	C	D
0	0	0	0
0	0	1	1
0	1	0	0
1	0	1	1
1	0	0	0

$$G_1 \rightarrow \rightarrow \bar{A}\bar{C}$$

$$G_2 \rightarrow \rightarrow \bar{A}B$$

$$G_3 \rightarrow \rightarrow \bar{B}\bar{C}\bar{D}$$


$$G_4 \rightarrow \rightarrow A\bar{B}\bar{C}\bar{D}$$

$$Q. Y = \sum_m (0, 1, 2, 3, 4, 5, 6, 7, 9, 11, 12, 13, 14, 15)$$

Step ①: $2^n = 15 \simeq 16$


$\therefore n = 4$

Step -②:

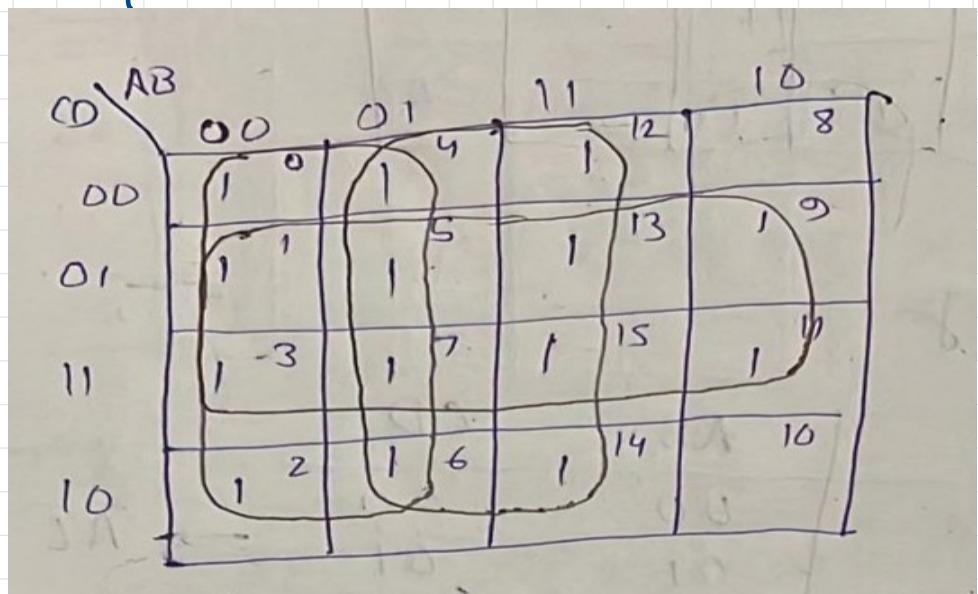

Step -③: Grouping on K-Map.

Step -④:

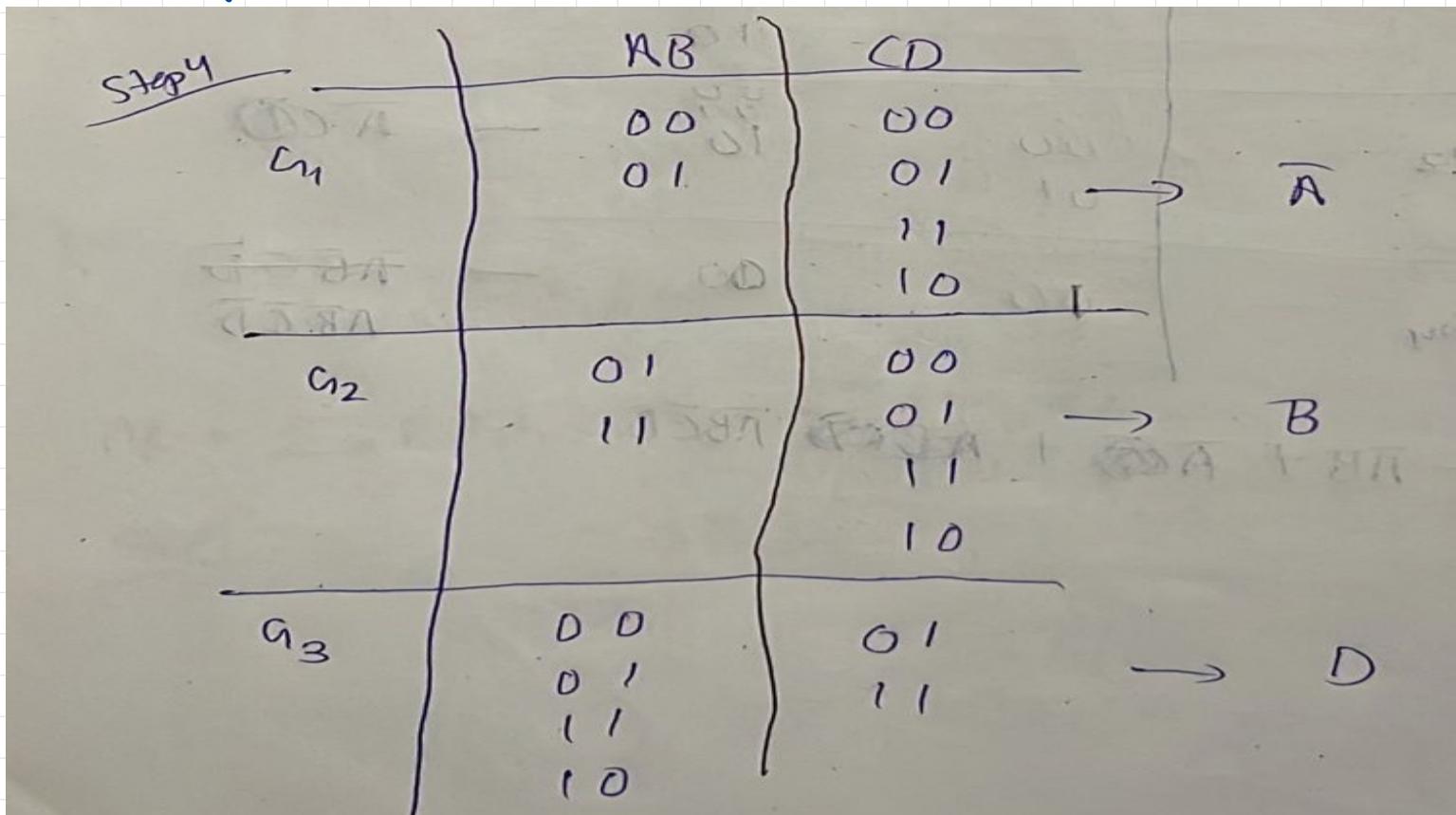


$$Q. Y = \sum_m (3, 4, 5, 7, 9, 13, 14, 15)$$

REMEMBER

Soln: $2^n = 15 \simeq 16 \Rightarrow n = 4$



Special Care

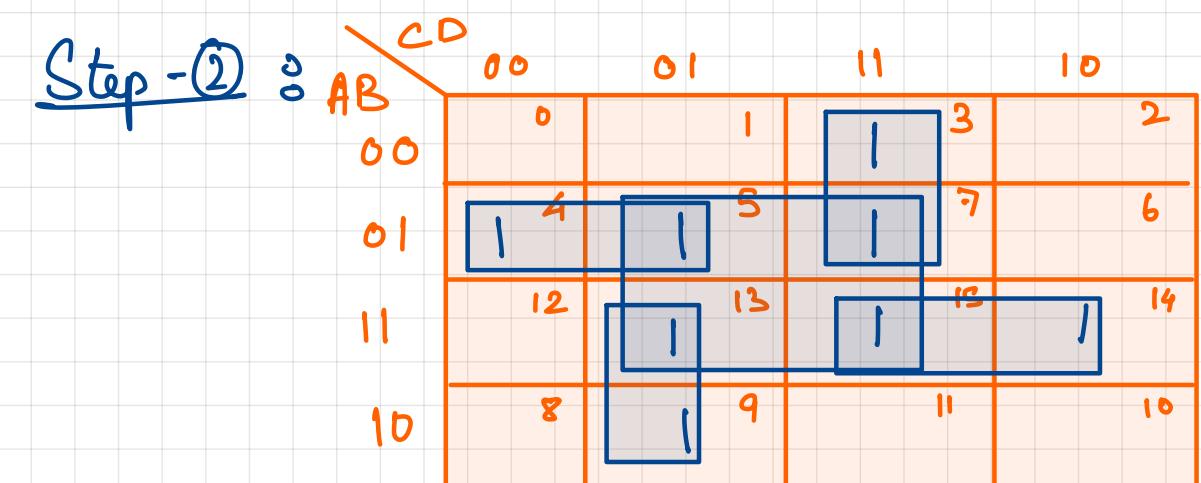

Here all the 4 1's covered by quad group are also covered by pair. So the quad grouping will be ignored.

Step - 3: Grouping



Step - ④ :

$$G_1 \rightarrow \begin{array}{c|c|c|c} A & B & C & D \\ \hline 0 & 0 & 1 & 1 \\ 0 & 1 & 1 & 1 \end{array} \rightarrow \bar{A}CD$$

$$G_2 \rightarrow \begin{array}{c|c|c|c} A & B & C & D \\ \hline 0 & 1 & 0 & 0 \\ 0 & 1 & 0 & 1 \end{array} \rightarrow \bar{A}B\bar{C}$$

$$G_3 \rightarrow \begin{array}{c|c|c|c} A & B & C & D \\ \hline 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 0 \end{array} \rightarrow ABC$$

$$G_4 \rightarrow \begin{array}{c|c|c|c} A & B & C & D \\ \hline 1 & 1 & 0 & 1 \\ 1 & 0 & 0 & 1 \end{array} \rightarrow A\bar{C}D$$

$$\begin{aligned} Y = & \bar{A}CD + \bar{A}B\bar{C} \\ & + ABC \\ & + A\bar{C}D \end{aligned}$$

• POS

$$1) Y = \pi(3, 4, 6, 7, 11, 12, 13, 14, 15)$$

$$2) Y = \pi(0, 1, 4, 5, 6, 8, 9, 12, 13, 14)$$


24/Sep/2022

Soln ①

Step ① : $2^k = 15 \approx 16$

$$k = 4$$

Step - ② :

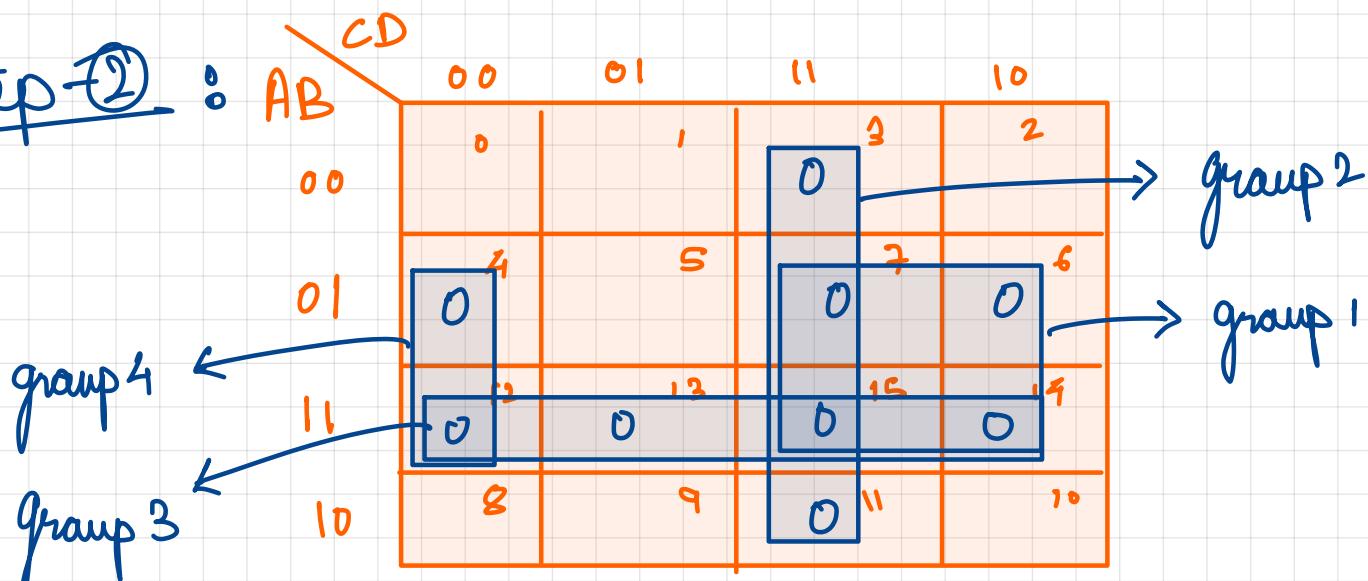

Step - ③ : Grouping on K-Map.

$$G_4 \rightarrow \begin{array}{c|c|c|c} A & B & C & D \\ \hline 0 & 1 & 0 & 0 \\ 1 & 1 & 0 & 0 \end{array} \rightarrow \bar{B} + C + D$$

Step - ④ :

$$G_1 \rightarrow \begin{array}{c|c|c|c} A & B & C & D \\ \hline 0 & 1 & 1 & 1 \\ 0 & 1 & 1 & 0 \end{array} \rightarrow \bar{B} + \bar{C}$$

$$\begin{aligned} \therefore Y = & (\bar{B} + \bar{C})(\bar{C} + \bar{D}) \\ & (A + \bar{B})(\bar{B} + C + D) \end{aligned}$$

$G_2 \rightarrow$

$$\begin{array}{c|c|c|c} A & B & C & D \\ \hline 0 & 0 & 1 & 1 \\ 1 & 1 & 1 & 1 \end{array} \rightarrow \bar{C} + \bar{D}$$

$G_3 \rightarrow$


$$\begin{array}{c|c|c|c} A & B & C & D \\ \hline 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 0 \end{array} \rightarrow \bar{A} + \bar{B}$$

Pm

②

$$\text{Step-①: } 2^n = 14 \simeq 16$$

$$n = 4$$

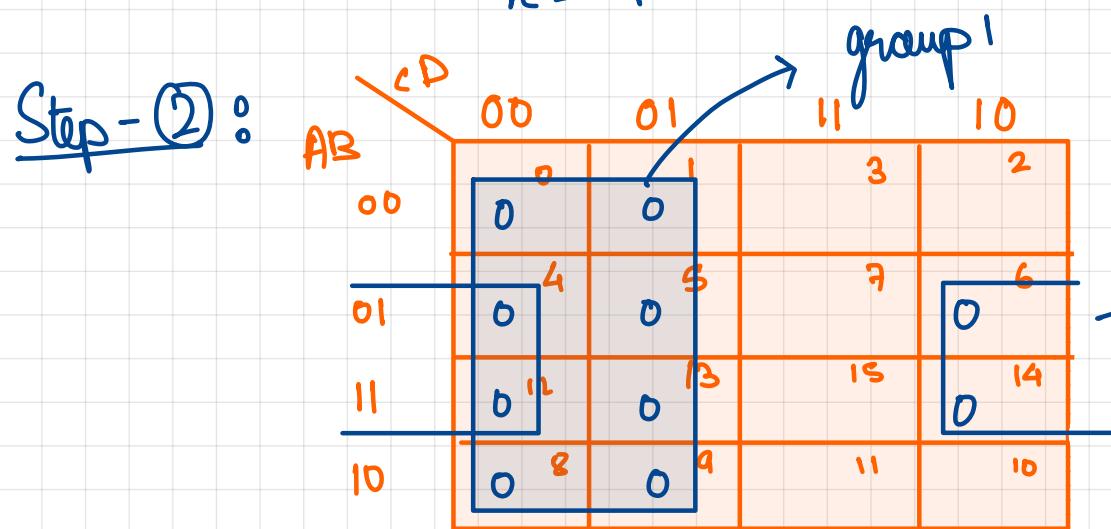

Step③: Grouping on K-Map.

Step-④:

$G_{1,1} \rightarrow$

A	B	C	D
0	0	0	0
0	0	0	1
0	1	0	0
0	1	0	1
1	1	0	0
1	1	0	1
1	0	0	0
1	0	0	1

$\rightarrow C$

∴

$$Y = C \cdot (\bar{B} + D)$$

$G_{1,2} \rightarrow$

	0	1	0	0
	0	1	1	0
	1	1	0	0
	1	1	1	0

$\rightarrow (\bar{B} + D)$

$$Y = \pi(0, 2, 4, 6, 8, 10, 12, 14)$$

Step③: Grouping

Step-④:


A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	1	1	0
1	0	0	0
1	0	1	0

$\Rightarrow D$

Step-②:

$G_{1,1} \rightarrow$

$n = 4$

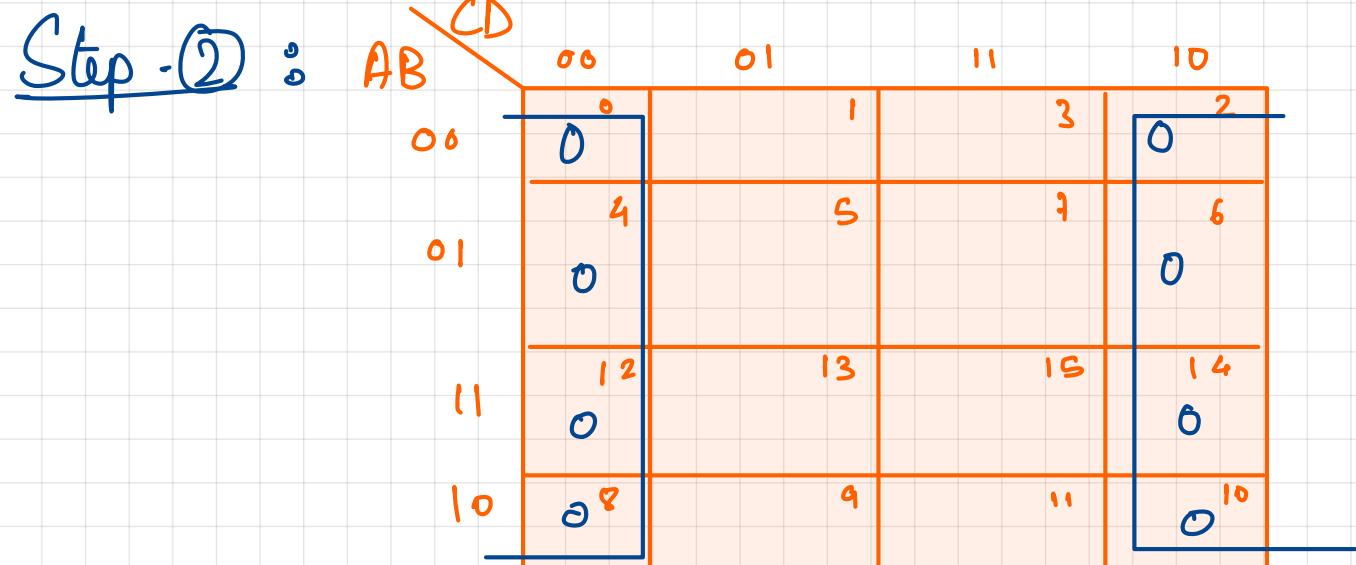

$$\therefore Y = D$$

Don't Care Condition :-

- Usually we are representing the don't care form as 'd' or 'x'.
- Objective : Not to take all the don't care form available in the K-Map table.
- We should take the combination of 1's and don't care 'd' (SOP) and the combination of 0's & 'd' in (POS), when it covers maximum number of 1's (SOP) & 0's (POS) in the adjacent cell.
- For SOP when we will take the don't care form along with the 1's to make a group then 'd' will be treated as 1 and for POS 'd' will be treated as 0.

$$Y = \sum_m (1, 3, 7, 11, 15) + \sum_d (0, 2, 5)$$

AB \ CD

	00	01	11	10	
00	d 0	1 1	1 3	d 2	G_1
01	4	d 5	1 7	6	G_2
11	12	13	1 15	14	
10	8	9	11	10	

A	B	C	D
$G_1 \rightarrow 0$	0	:	:
		:	$\rightarrow \bar{A}\bar{B}$
$G_2 \rightarrow :$:	1	1 $\rightarrow CD$
$\therefore Y = \bar{A}\bar{B} + CD$			

$$Y = \pi(0, 1, 2, 3, 8, 9, 11) + \sum_d(5, 10, 15)$$

AB \ CD


	00	01	11	10	
00	0 0	0 1	0 3	0 2	
01	4	d 5	7	6	
11	12	13	d 15	14	
10	0 8	0 9	0 11	d 10	

A	B	C	D
0	0	0	0
		:	:
1	0	0	0
		:	$\rightarrow B$

$$\therefore Y = B$$

• De Multiplexer :- (DeMUX)

03/Nov/2022

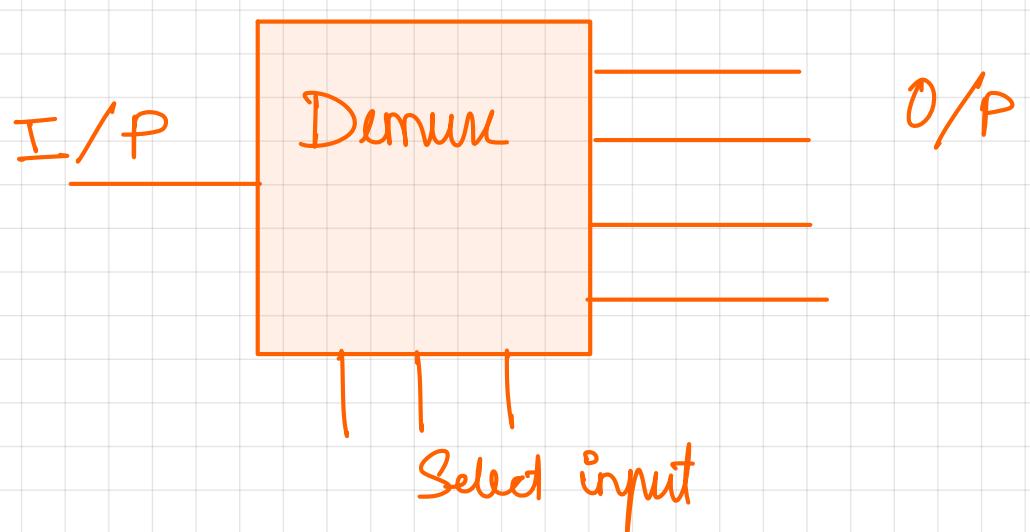

$$2^m = n$$

m = Select input

n = Output




1 : 4

Truth Table

Data I/P (D)	Select I/P (S ₀)	Select I/P (S ₁)	O/P Y ₀ Y ₁ Y ₂ Y ₃
D	0	0	D 0 0 0
D	0	1	0 D 0 0
D	1	0	0 0 D 0
D	1	1	0 0 0 D

$$Y_0 = D \bar{S}_0 \bar{S}_1, \quad Y_2 = D S_0 \bar{S}_1$$
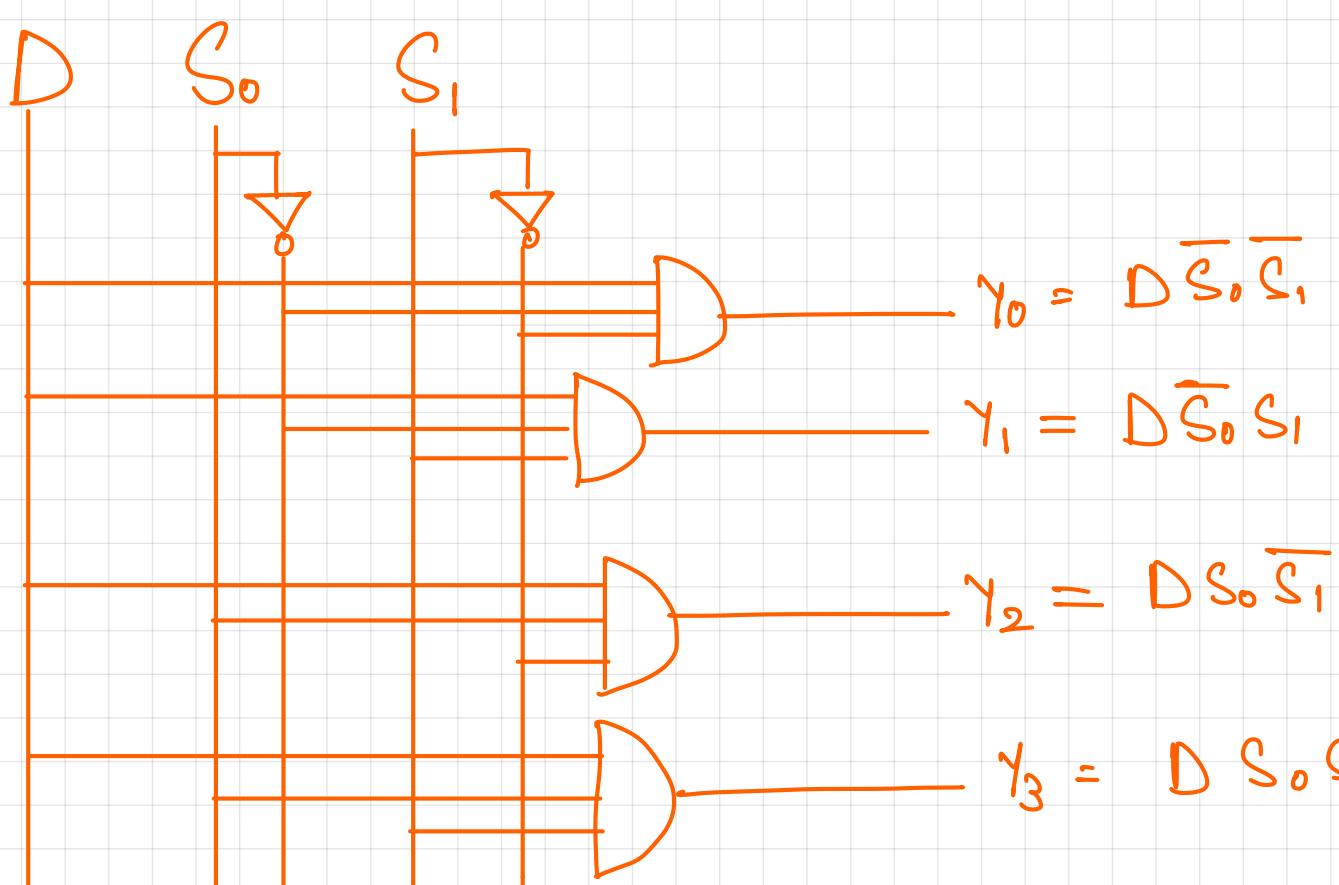
$$Y_1 = D \bar{S}_0 S_1, \quad Y_3 = D S_0 S_1$$



$$Y_0 = D \bar{S}_0 \bar{S}_1$$

$$Y_1 = D \bar{S}_0 S_1$$

$$Y_2 = D S_0 \bar{S}_1$$


$$Y_3 = D S_0 S_1$$

$$Y_5 = D S_0 \bar{S}_1 \bar{S}_2$$

$$Y_6 = D S_0 S_1 \bar{S}_2$$

$$Y_7 = D S_0 S_1 S_2$$

• 1 : 8 =

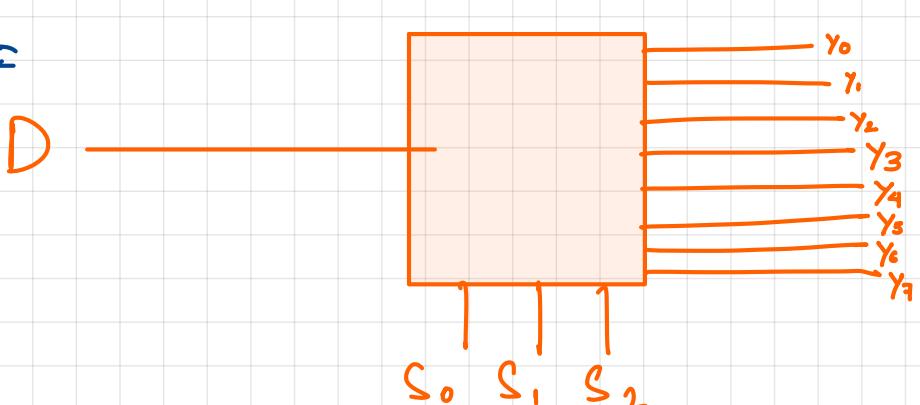

$$Y_0 = D \bar{S}_0 \bar{S}_1 \bar{S}_2$$

$$Y_6 = D S_0 \bar{S}_1 \bar{S}_2$$


$$Y_7 = D S_0 S_1 \bar{S}_2$$

$$Y_3 = D \bar{S}_0 S_1 \bar{S}_2$$



$$Y_4 = D S_0 \bar{S}_1 \bar{S}_2$$

• Truth Table :-

D(F/P)	S_0	S_1	S_2	y_0	y_1	y_2	y_3	y_4	y_5	y_6	y_7
D	0	0	0	D	0	0	0	0	0	0	0
D	0	0	1	0	D	0	0	0	0	0	0
D	0	1	0	0	0	0	D	0	0	0	0
D	0	1	1	0	0	0	D	0	0	0	0
D	1	0	0	0	0	0	0	D	0	0	0
D	1	0	1	0	0	0	0	0	D	0	0
D	1	1	0	0	0	0	0	0	0	D	0
D	1	1	1	0	0	0	0	0	0	0	D

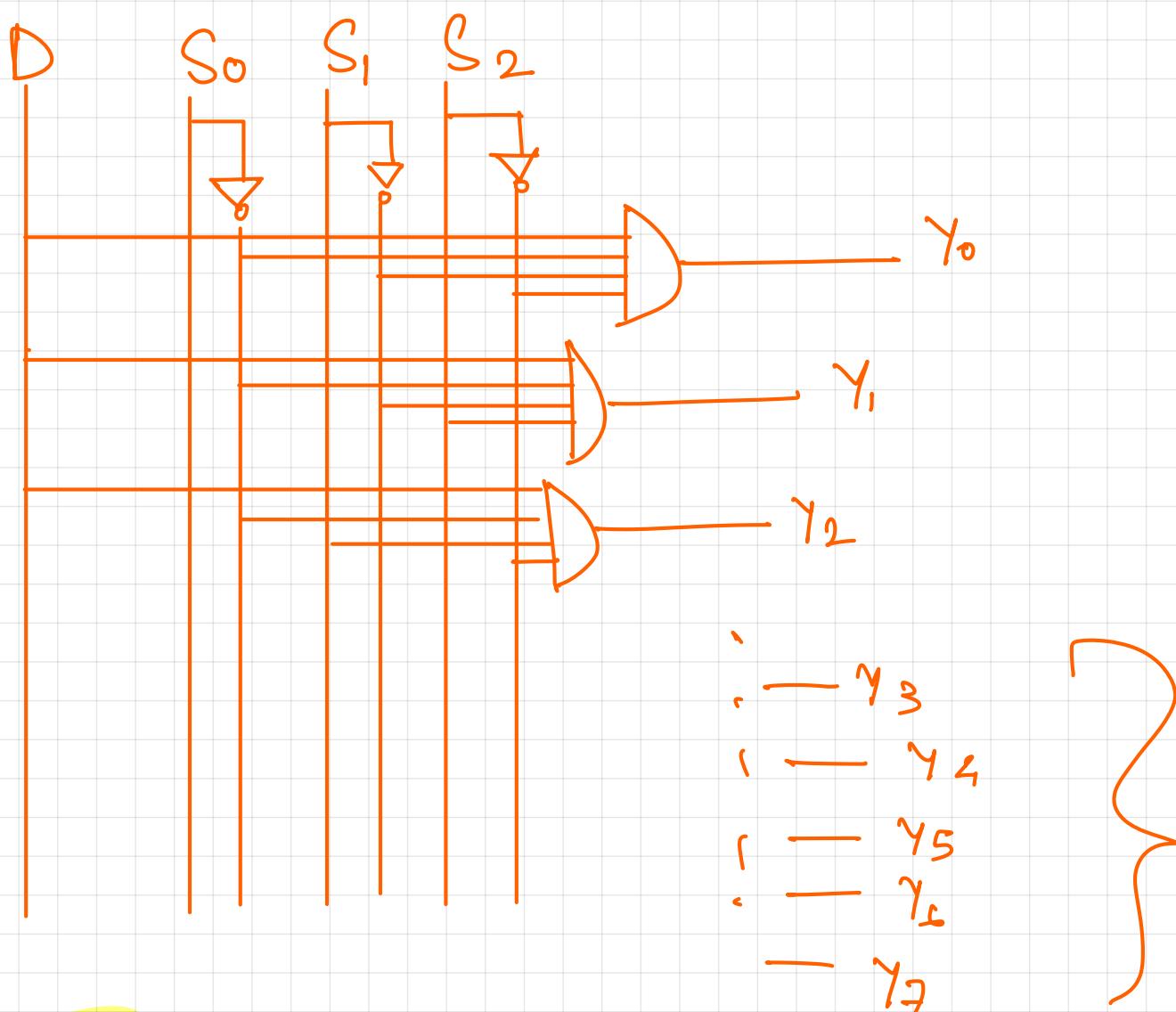

• Decoder :-

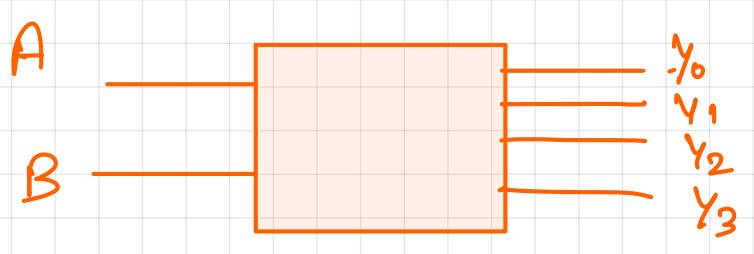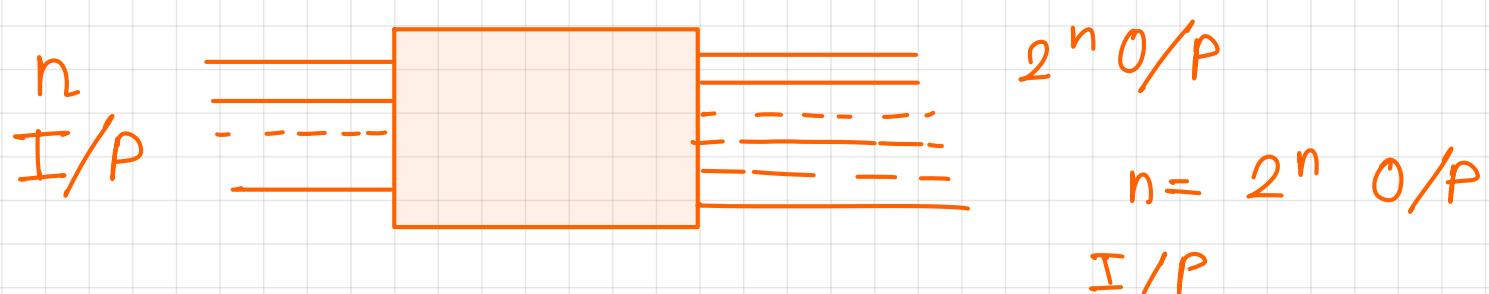

Decode \rightarrow code \rightarrow original
Encode \rightarrow original \rightarrow code

• Truth Table


I/P		O/P			
A	B	y_0	y_1	y_2	y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

$$y_0 = \overline{A}\overline{B}$$


$$y_1 = \overline{A}B$$

$$y_2 = A\overline{B}$$

$$y_3 = AB$$

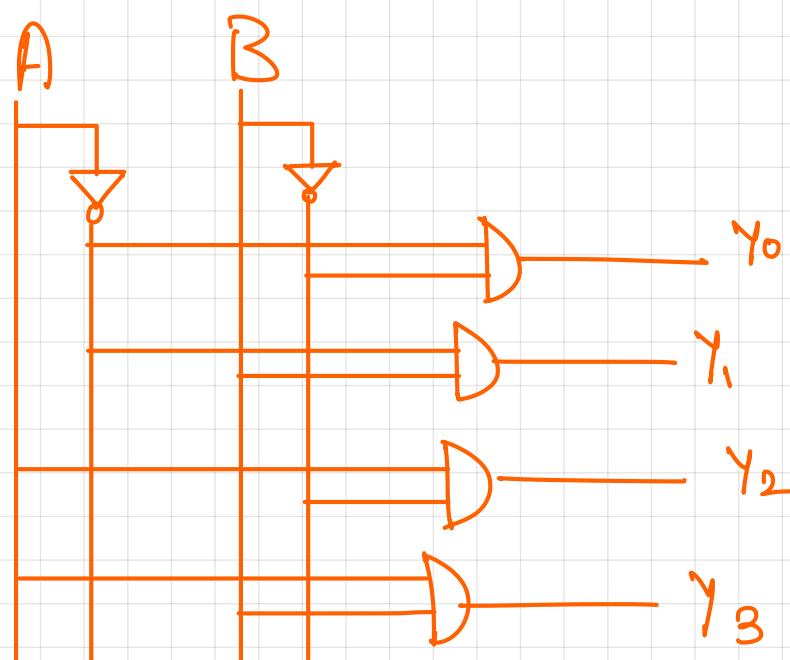

• Encoder :-

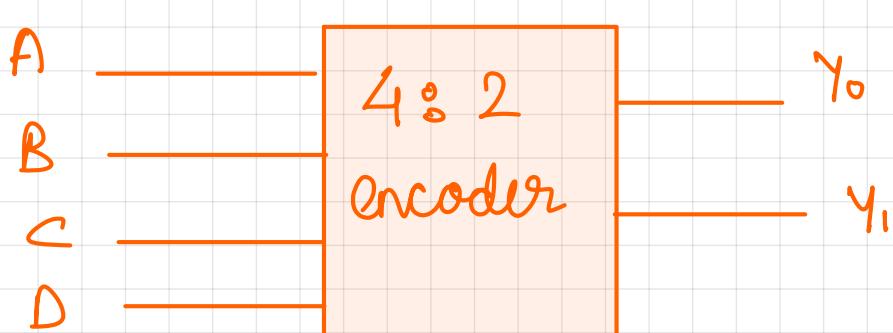

$$n = O/P$$


$$2^n = I/P$$


Truth Table :-

I/P				O/P	
A	B	C	D	y_0	y_1
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

$$y_0 = C+D$$


$$y_1 = B+D$$

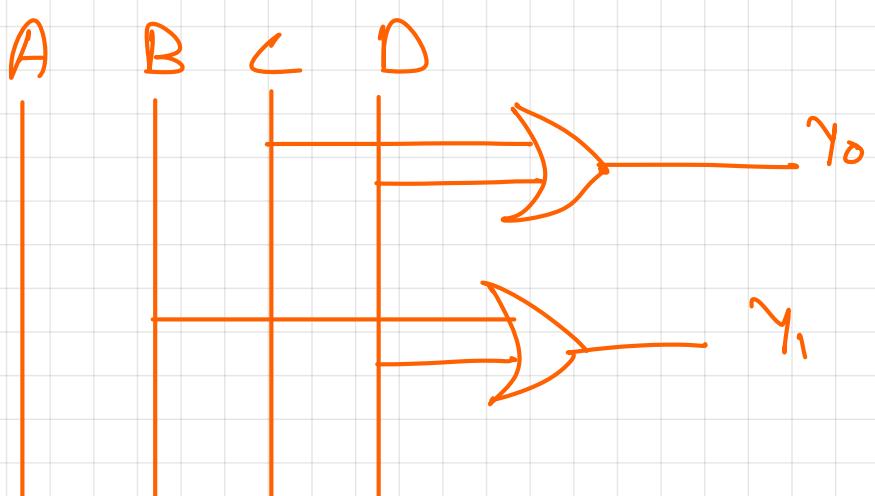

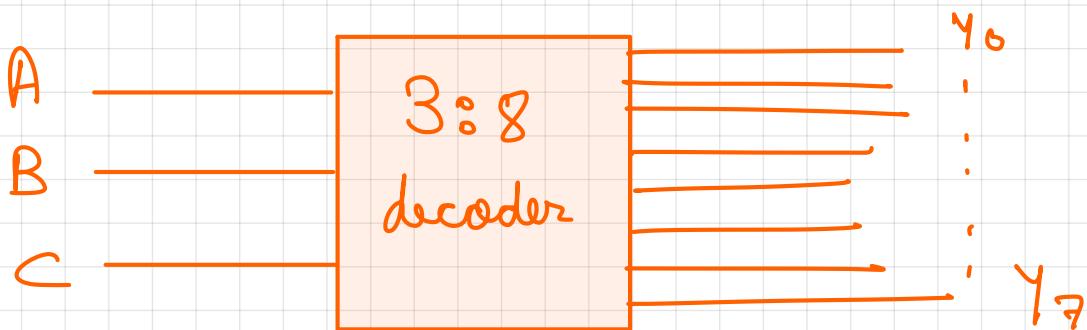


Input	A	B	C	Output	y_0	y_1	y_2	y_3	y_4	y_5	y_6	y_7	
000	0	0	0		1	0	0	0	0	0	0	0	0
001	0	0	1		0	1	0	0	0	0	0	0	0
010	0	1	0		0	0	1	0	0	0	0	0	0
011	0	1	1		0	0	0	1	0	0	0	0	0
100	1	0	0		0	0	0	0	1	0	0	0	0
101	1	0	1		0	0	0	0	0	1	0	0	0
110	1	1	0		0	0	0	0	0	0	1	0	0
111	1	1	1		0	0	0	0	0	0	0	1	0
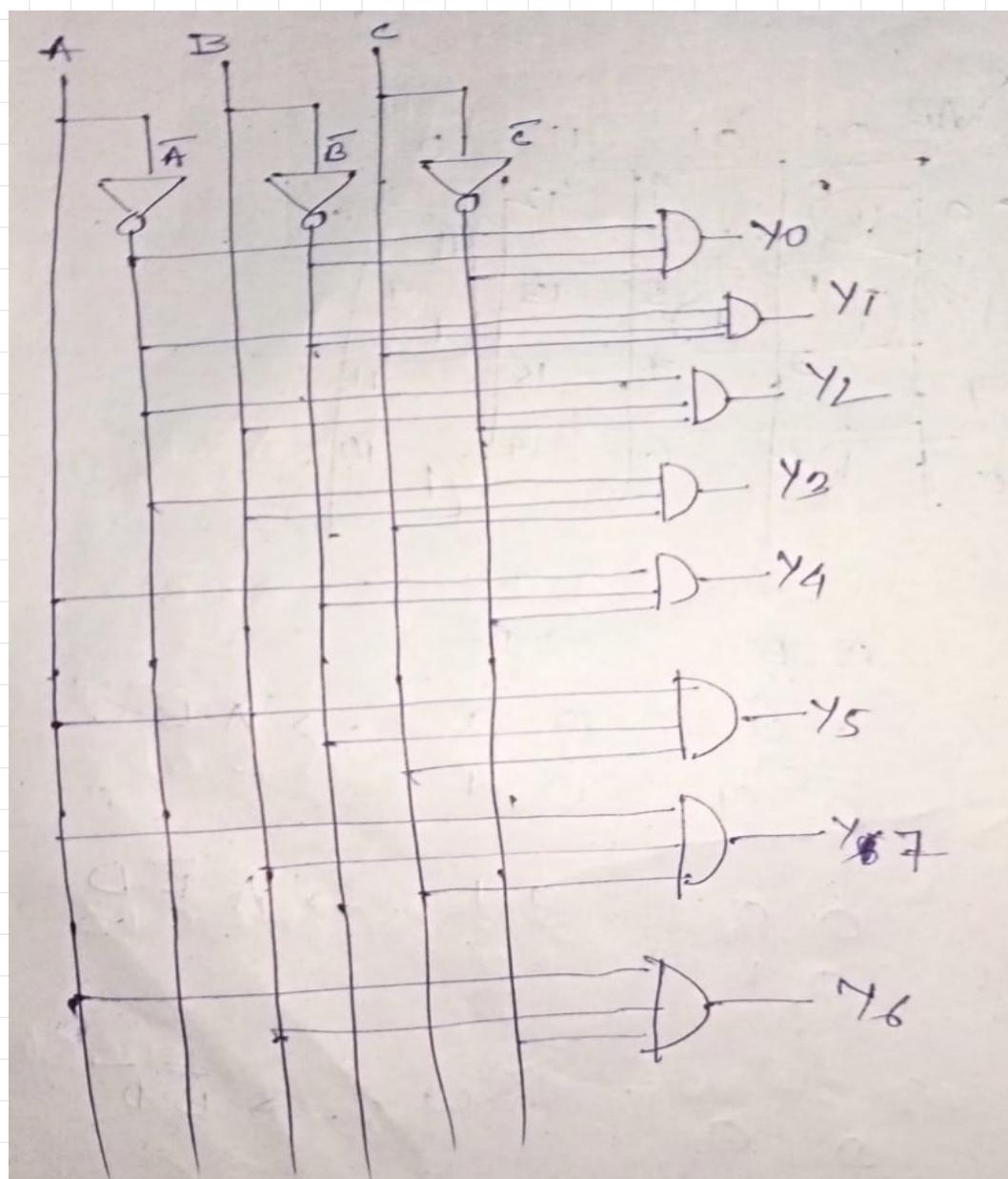
$$\Rightarrow \begin{aligned} y_0 &= \bar{A}\bar{B}\bar{C} & y_5 &= A\bar{B}\bar{C} \\ y_1 &= \bar{A}\bar{B}C & y_6 &= AB\bar{C} \\ y_2 &= \bar{A}B\bar{C} & y_7 &= ABC \\ y_3 &= \bar{A}BC \\ y_4 &= A\bar{B}\bar{C} \end{aligned}$$



\Rightarrow logic diagram,

Encoder :-

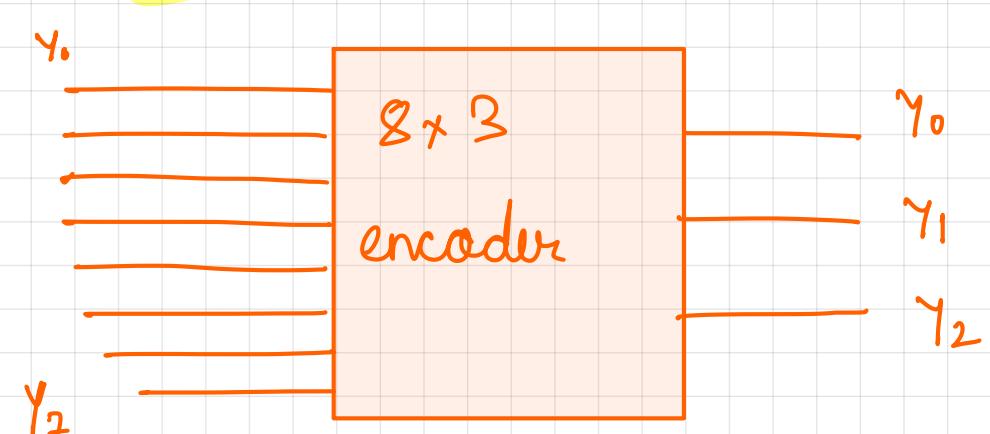


D/I	y_0	y_1	y_2	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	P/I	
00	0	0	0	1	0	0	0	0	0	0	0	0	0000
00	0	0	1	0	1	0	0	0	0	0	0	0	0000
01	0	1	0	0	0	1	0	0	0	0	0	0	0000
01	0	1	1	0	0	0	1	0	0	0	0	0	0000
10	1	0	0	0	0	0	0	1	0	0	0	0	0000
10	1	0	1	0	0	0	0	1	0	0	0	0	0000
11	1	1	0	0	0	0	0	0	1	0	0	0	0000
11	1	1	1	0	0	0	0	0	0	1	0	0	0000

$$y_0 = D_4 + D_5 + D_6 + D_7$$

$$y_1 = D_2 + D_3 + D_6 + D_7$$

$$y_2 = D_1 + D_3 + D_5 + D_7$$

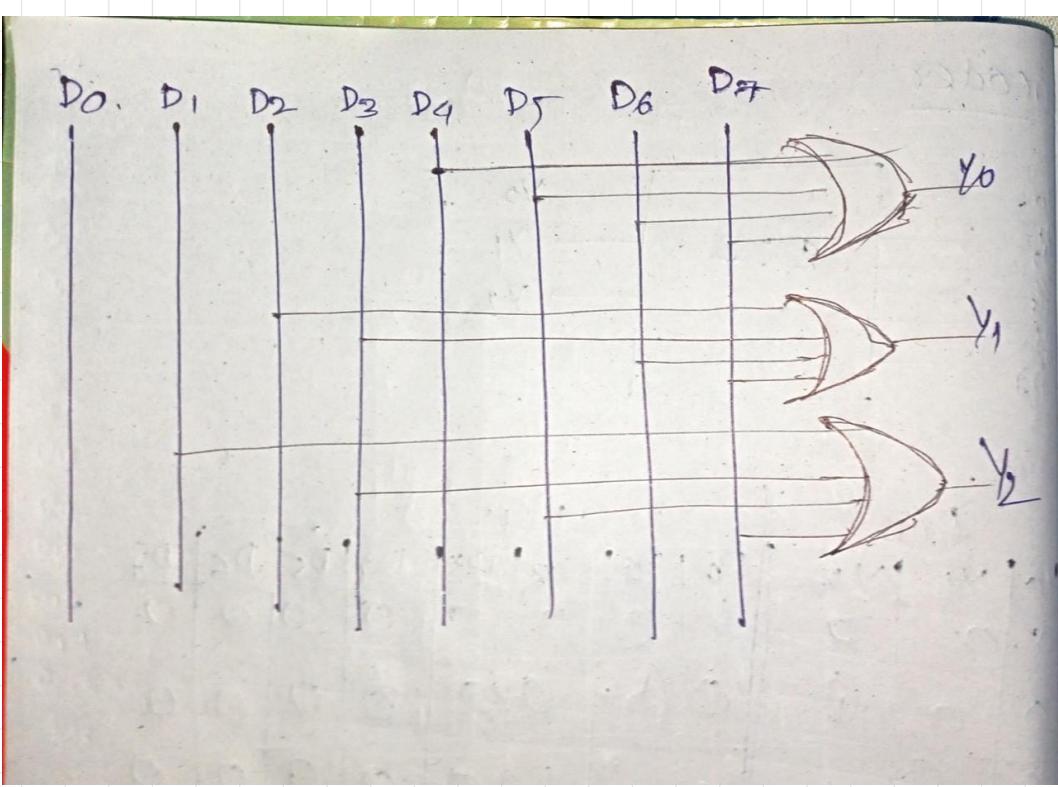


• J-K Flip Flop :-


11/Nov/2022,

Symbol


CLK

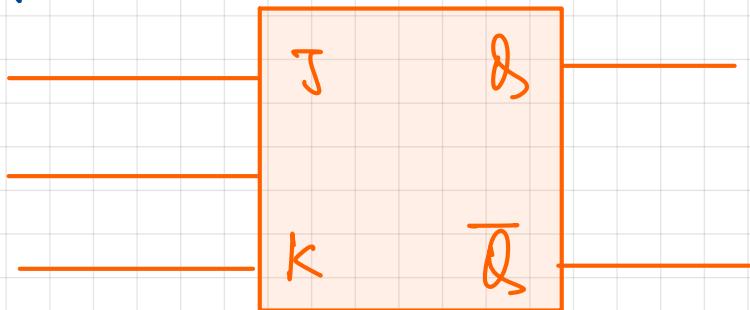

Block diagram :-

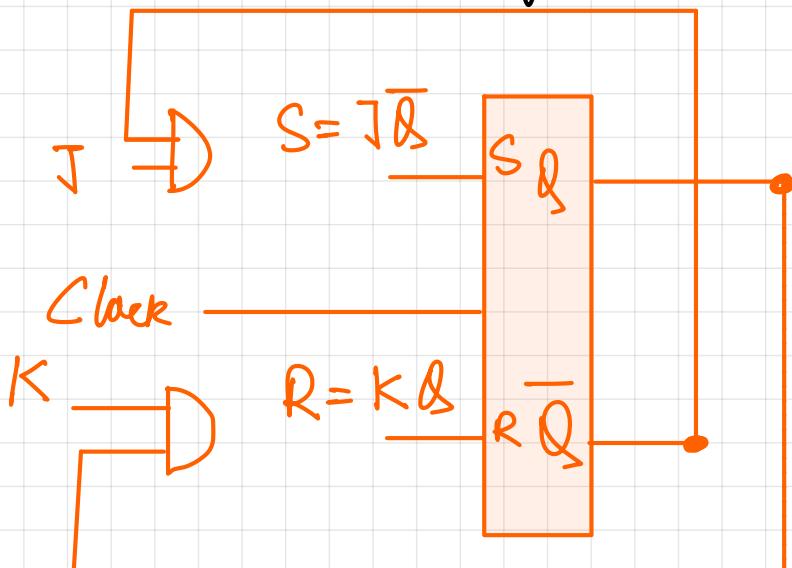


Circuit diagram :-

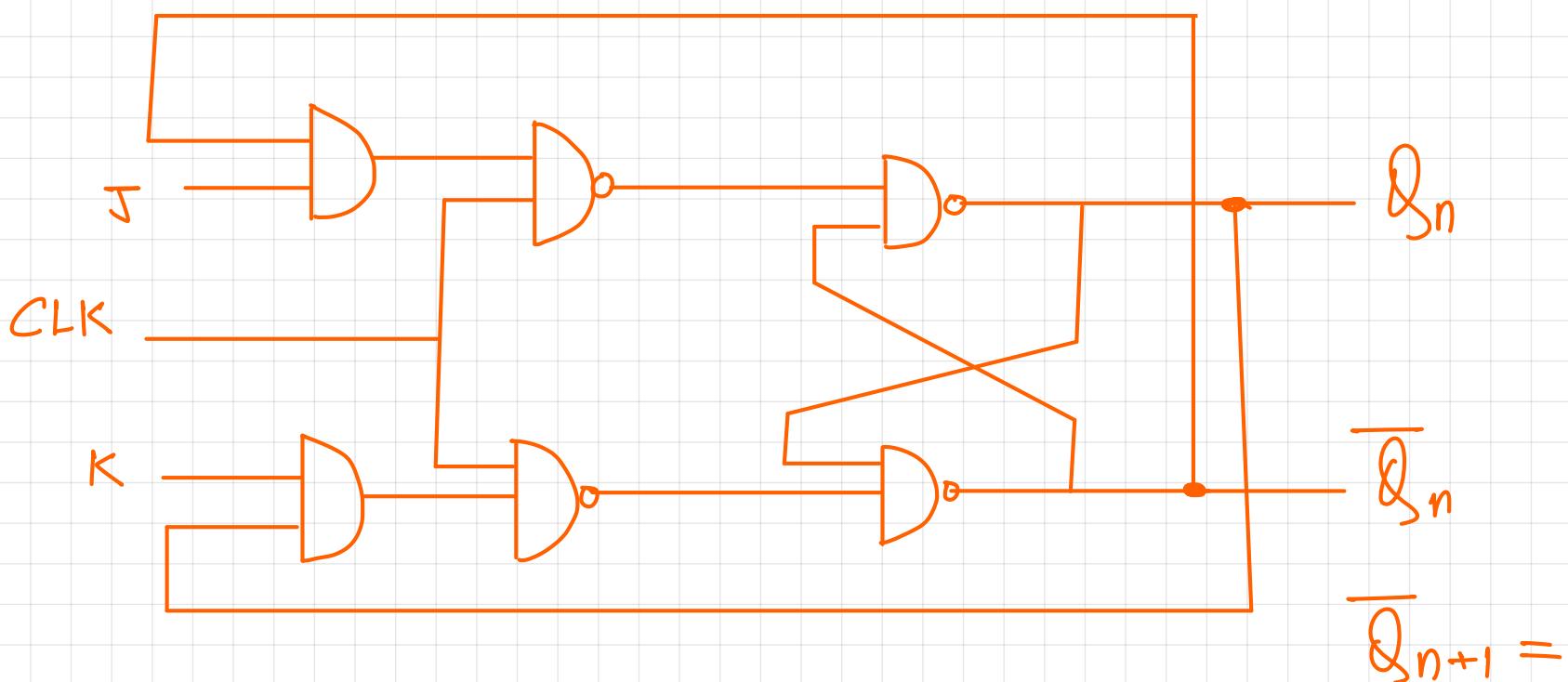


Truth Table :-

CLK	Q_n	J K	Q_{n+1}	\bar{Q}_{n+1}	Action
1	0/1	0 0	Q_n	\bar{Q}_n	No change
1	0/1	0 1	0	1	Reset
1	0/1	1 0	1	0	Set
1	0/1	1 1	1/0	0/1	Toggle
0	0/1	0 0			
0	0/1	0 1			
0	0/1	1 0			
0	0/1	1 1			

② Race Around Condition

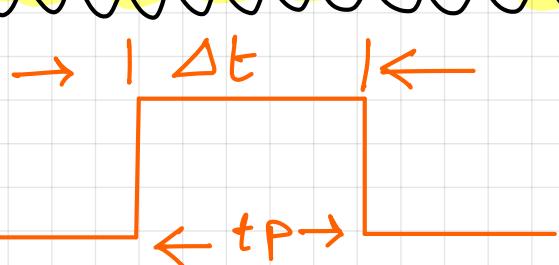

$$\Delta t < \Delta t_p$$

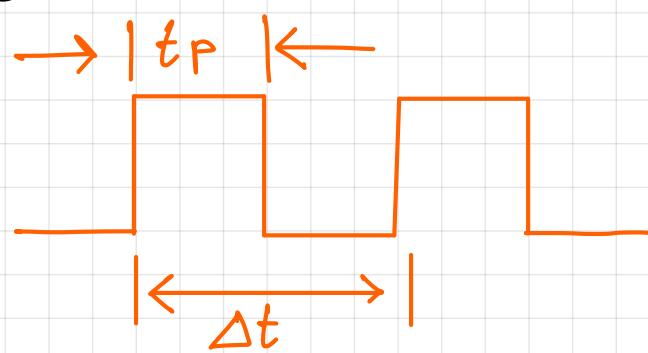

$$\Delta t > t_p$$

t_p = width of clock pulse

Δt = propagation delay.

When, $J = K = 1$

After one propagation delay the output of J-K flip flop is 1. ($Q_n = 0$)


After another propagation time period the O/P of flip flop is 0.

When, $J = K = 1$, $Q_n = 0$ then $Q_{n+1} = 1$

$J = K = 1$, $Q_n = 1$ then $Q_{n+1} = 0$

When, $J = K = 1$

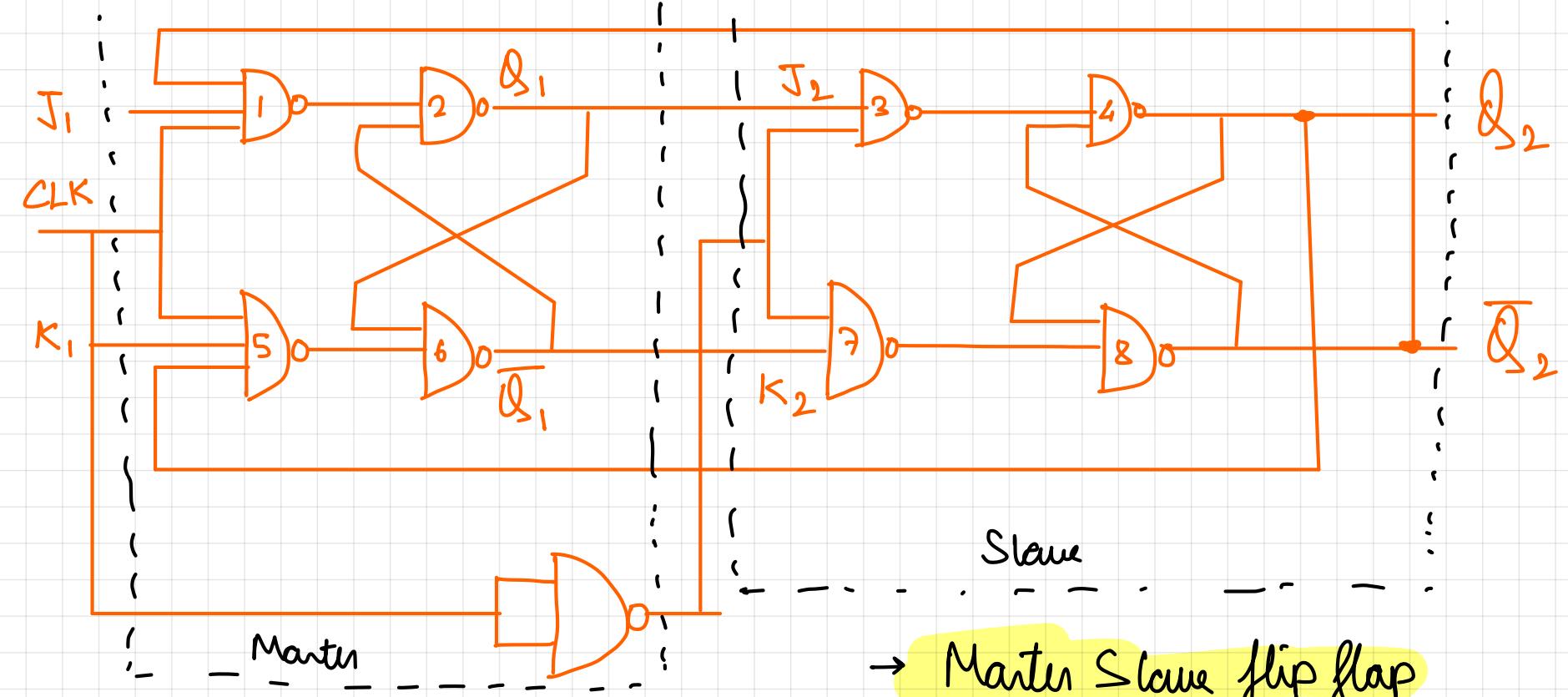So within the width of clock pulse both the O/P of J-K flip flop are changing.



→ Master Slave flip flop


- Using 2 JK flip flops the master slave flip flop can be constructed.
- The 2 J-K flip flops are connected in series.
- 4 NAND are used to make master flip flop another 4 NAND used to make slave flip flop.
- The master flip flop is triggered at the positive edge of the clock pulse. And the slave flip flop is triggered at negative edge of clock pulse.
- When $J_1 = 1, K_1 = 0$, the output of the master flip flop (Q_1) = 1 (at positive edge of clock pulse). The output $Q_1 = 1$ drives the input J_2 of the slave flip flop. At the negative edge of clock pulse the slave flip flop will copy the action of master flip flop.

MASTER-SLAVE

10/Nov/2022

Latch :-

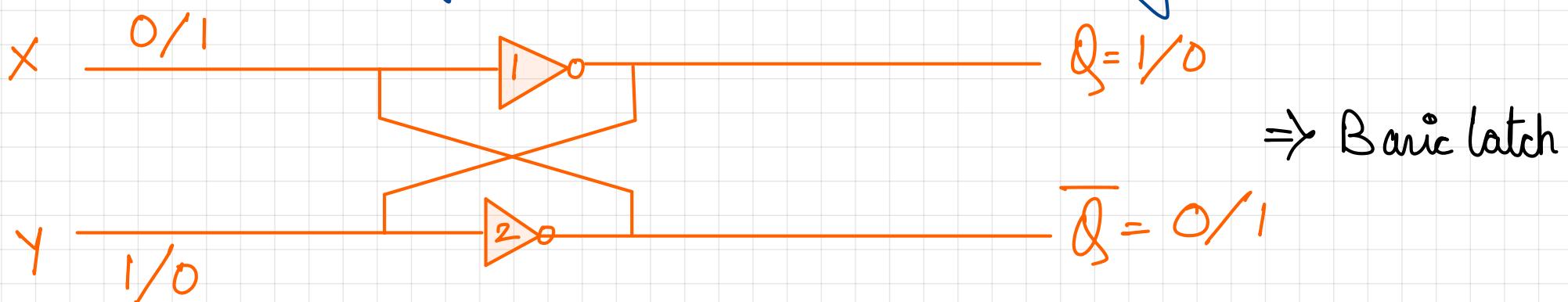
Both the O/P of two inverters are complementary to each other



- The simplest kind of sequential circuit, has only two states
- 1 bit of info is stored.
- logic 0 or logic 1

NOR-based Set-Reset latch (S-R latch) :-


→ Block diagram

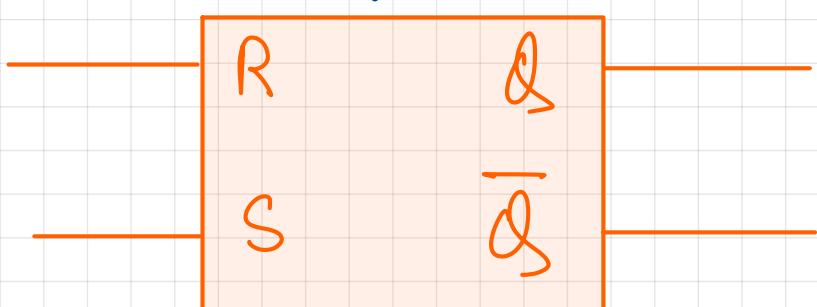

→ Truth Table

S	R	Q_{n+1}	\bar{Q}_{n+1}	Action
0	0	0/1/ Q_n	1/0/ \bar{Q}_n	No change
0	1	0	1	Reset
1	0	1	0	Set
1	1	?	?	forbidden

→ Circuit diagram

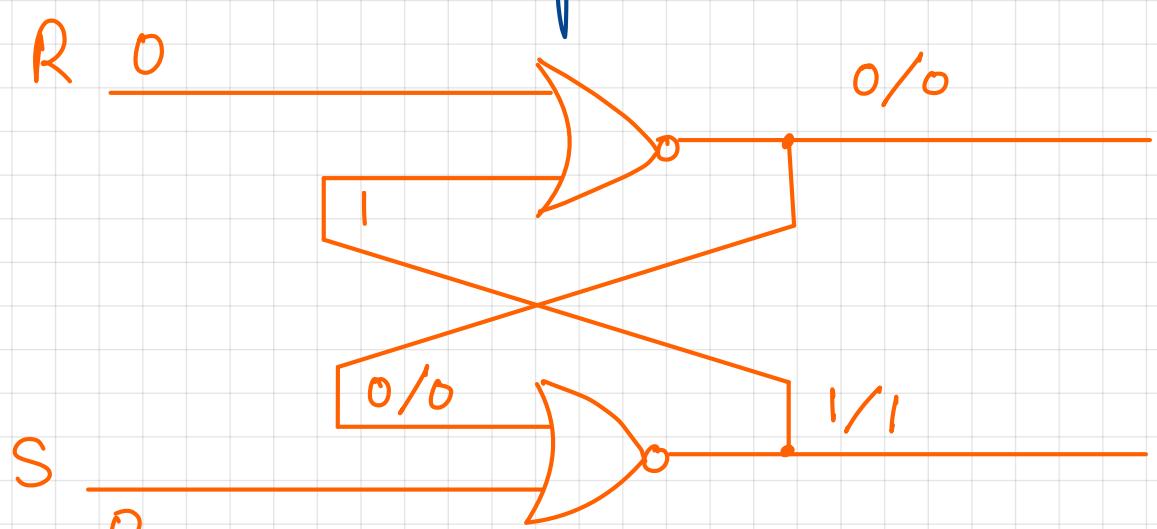

$Q_n \rightarrow$ Present state

$Q_{n+1} \rightarrow$ Complement of present state

$\bar{Q}_n \rightarrow$ Next state


$\bar{Q}_{n+1} \rightarrow$ Complement of next state.

• Flip Flops :-


- This is a Sequential Circuit.
 - If we provide an additional control input to the basic latch, then the state of the circuit will be changed.
 - The latch with the additional control input is called flip flop.
 - The additional control input may be clock or enable input.
-

• S-R flip flop :-


→ Symbol

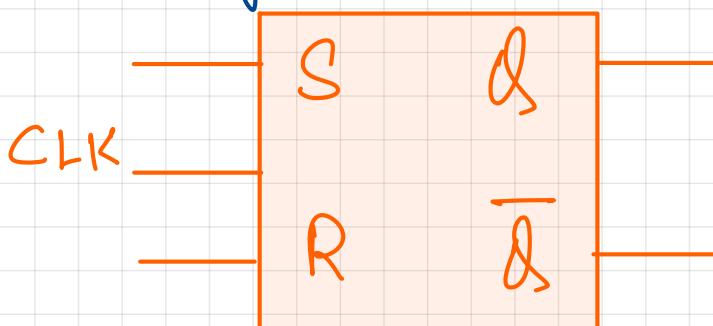

→ Block diagram

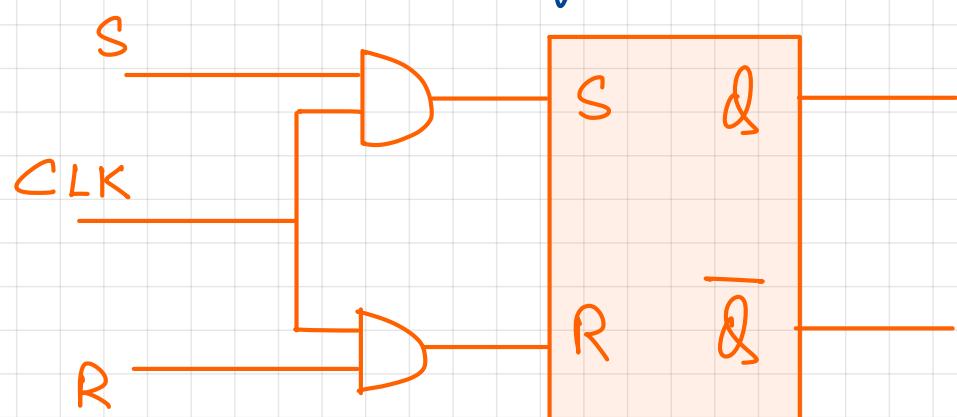

→ Circuit diagram

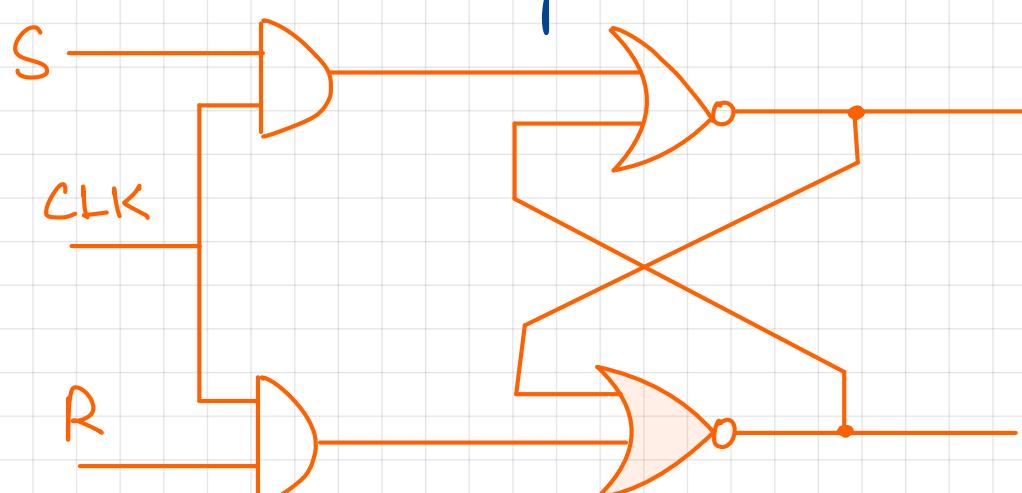



→ Truth Table

CLK	Q_n	S	R	Q_{n+1}	\bar{Q}_{n+1}	Action
1	0/1	0	0	0/1	1/0	No change
1	0/1	0	1	1	0	Set
1	0/1	1	0	0	1	Reset
1	0/1	1	1	?	?	forbidden
0	0/1	0	0	0/1	1/0	No change
0	0/1	0	1	0/1	1/0	No change
0	0/1	1	0	0/1	1/0	No change
0	0/1	1	1	0/1	1/0	No change.


• Delay flip-flops (D-flip flops)

→ Symbol

→ Using S-R flip flop

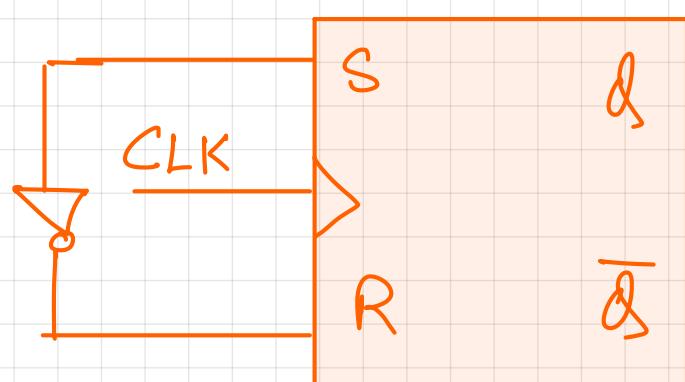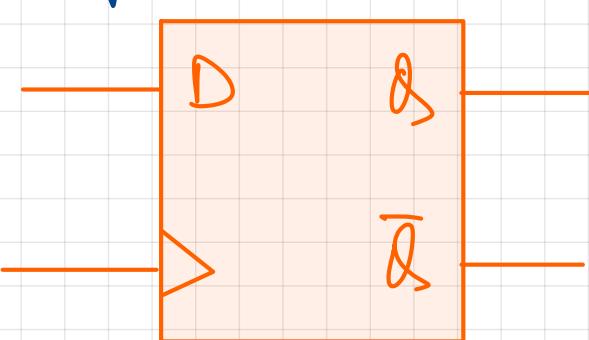

→ Circuit diagram

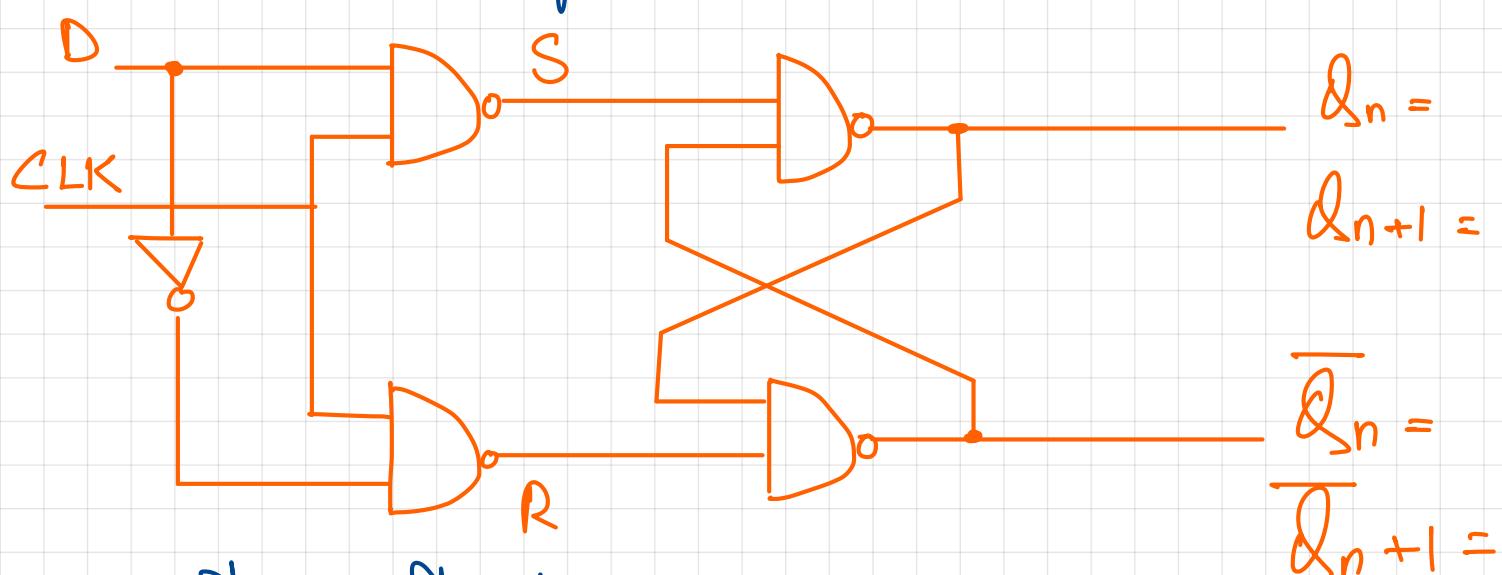

→ Truth Table

Q_n	CLK	D	Q_{n+1}
0/1	1	0	0
0/1	1	1	1
0/1	0	0	0
0/1	0	1	1

17/Nov/2022

- i) When $J_1=0$ $K_1=1$, the output of the master $Q_1=0$ and $Q'_1=1$, $Q'_1=1$, this will help to trigger the K_2 input of the slave flip flop.
- ii) At the negative edge of the clock pulse the slave flip flop will copy the same action of the master flip flop.
- iii) When $J_1=K_1=1$, the master flip flop toggles on the edge of the clock pulse & the slave flip flop toggles at the -ve edge of the clock pulse.

iv) When $J_1 = 0$ & $K_1 = 0$, the master and slave flip flop will remain at the same state.

Implementation of Boolean expression using multiplexer :-

$$F(A, B, C, D) = \sum(0, 1, 3, 4, 8, 9, 15)$$

$$(n+1) = 3+1$$

I/P of multiplexer

Selected input


BCD

$$A = A, \bar{A}, 0, 1$$

	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
\bar{A}	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	1	1	0	\bar{A}	\bar{A}	0	0	A

Rules :-

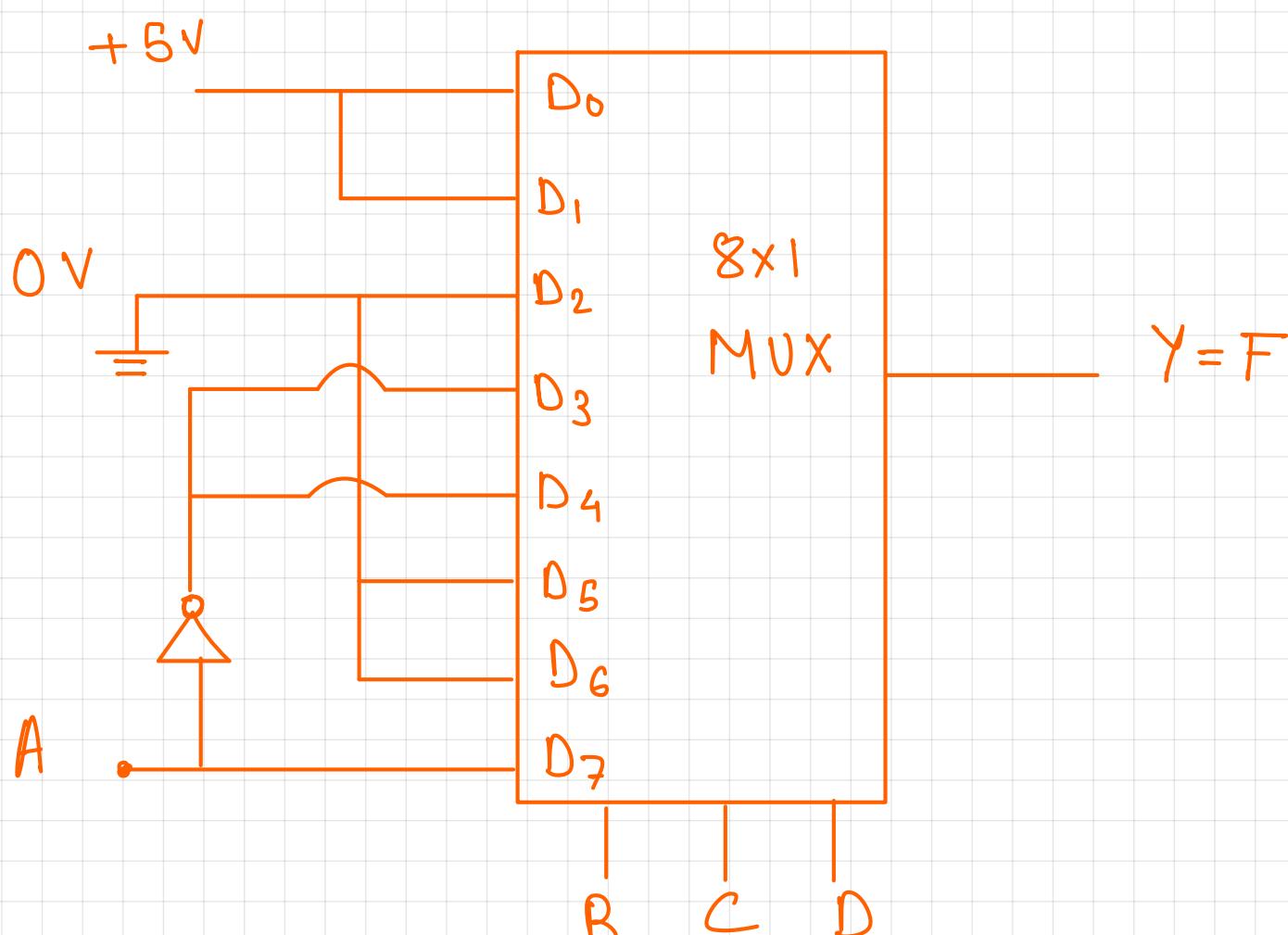- i) If both the minterms in a column are not circled apply 0 to the corresponding I/P.
- ii) If both the minterms in a column are circled apply 1 to the corresponding I/P.
- iii) If bottom minterm is circled and top is not circled apply A to the corresponding I/P.
- iv) If the top minterm is circled and the bottom is not, then apply \bar{A} to the corresponding I/P.




$$P(A, B, C) = \sum (1, 3, 5, 6)$$

$$(n+1) = 2+1$$

$B \quad C \quad A$

$$2^2 = 4$$

	D_0	D_1	D_2	D_3
\bar{A}	0	1	2	3
A	4	5	6	7
	0	1	A	\bar{A}

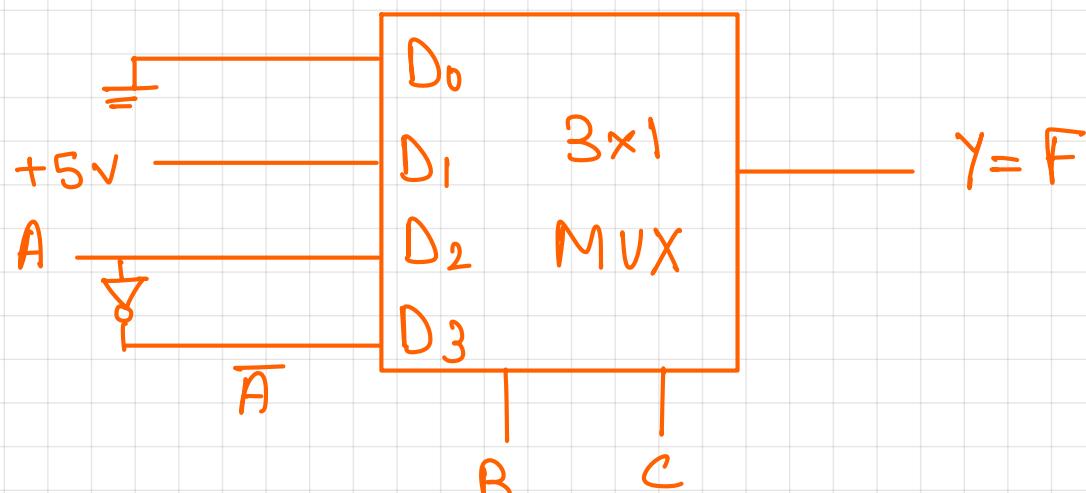


Counters

21 Nov / 2022

- i) If it is a sequential circuit.
- ii) It consists of flip flops.
- iii) Consists of binary input sequence in digital form.

Asynchronous counter — Speed ↓


+VCC

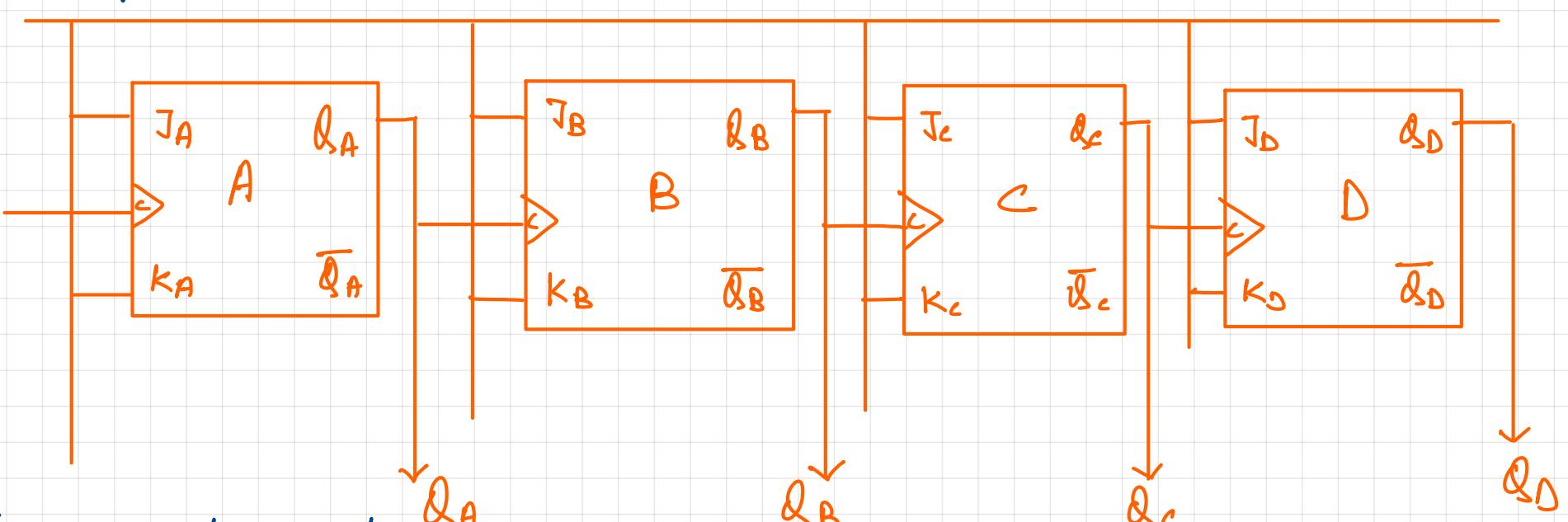

- i) A flip flop is triggered by clock input pulse.
- ii) B flip flop is triggered by the Q_A , output of A flip flop.
- iii) C flip flop is triggered by the Q_B , output of B flip flop.
- iv) D flip flop is triggered by the Q_C , output of C flip flop.
- v) All J-K input of A, B, C, D are connected with +VCC.
- vi) All flip flops are toggling, as $J=K=1$, at the -ve transition of clock pulse I/P.

Clock Pulse input :-

Initially $Q_A = Q_B = Q_C = Q_D = 0$

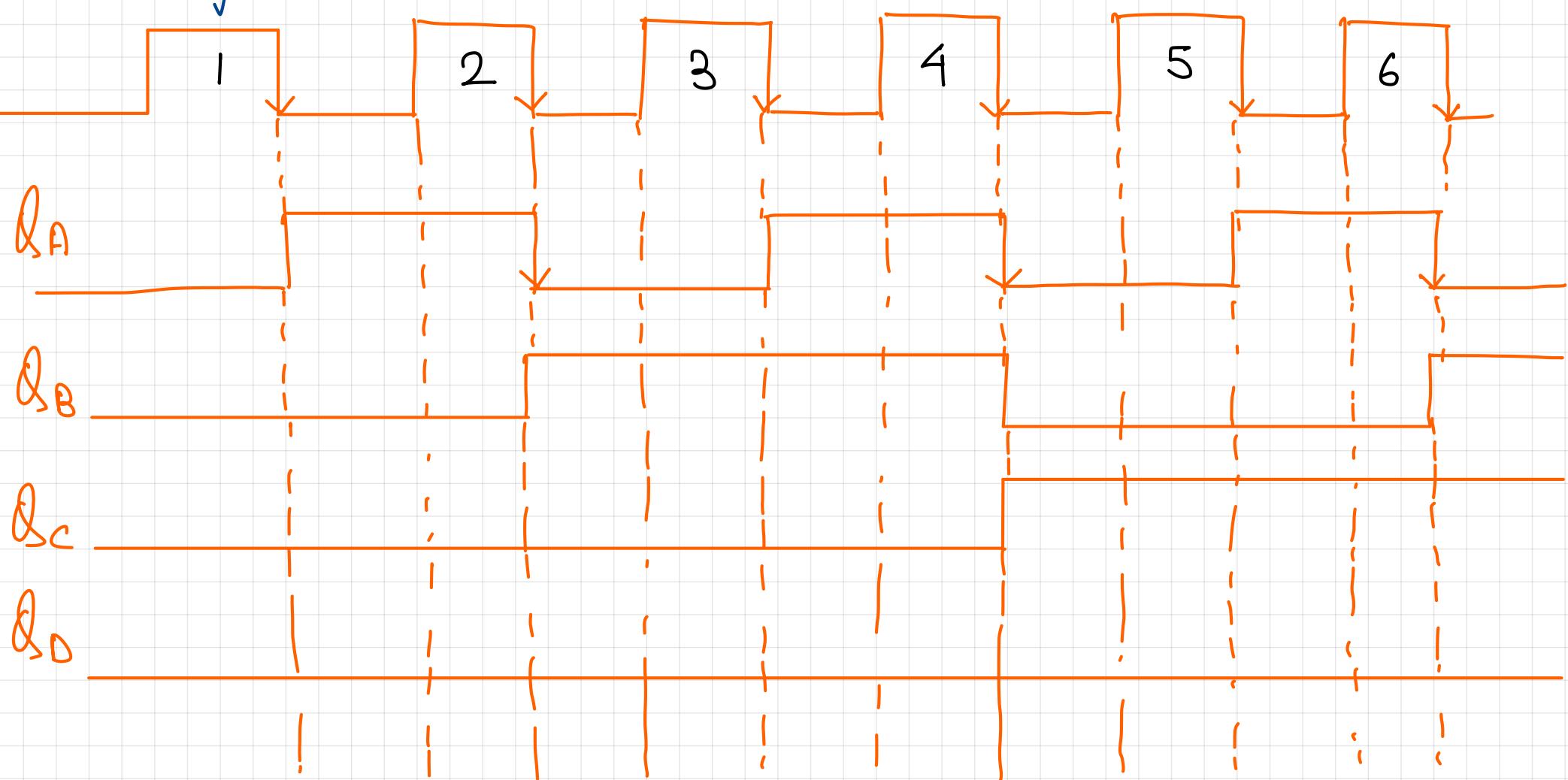

Truth Table :-

State	Q_D	Q_C	Q_B	Q_A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

• Register :-


Function : Registers consist a set of flip flops to store binary information in it.

Also registers can shift binary information from one side to another side.

There are 4 types of register :

- ① SISO (Serial In Serial Out)
- ② SIPO (Serial in Parallel Out)
- ③ PISO (Parallel in Serial Out)
- ④ PIPO (Parallel in Parallel Out)


■ SISO Register :-

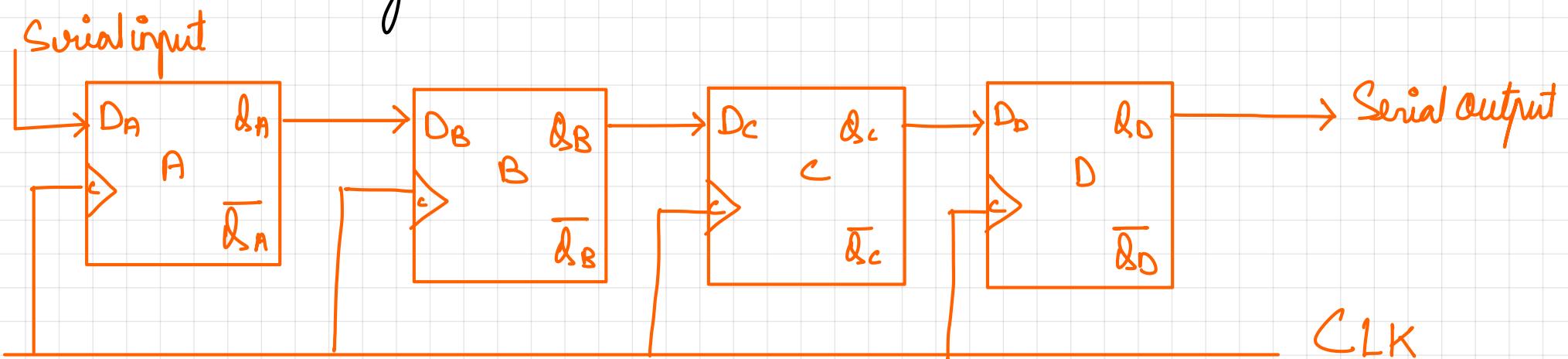


Truth Table :

CLK	Q _A	Q _B	Q _C	Q _D
X	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	0	1	1	0
4	1	0	1	1

SIPO Register :-

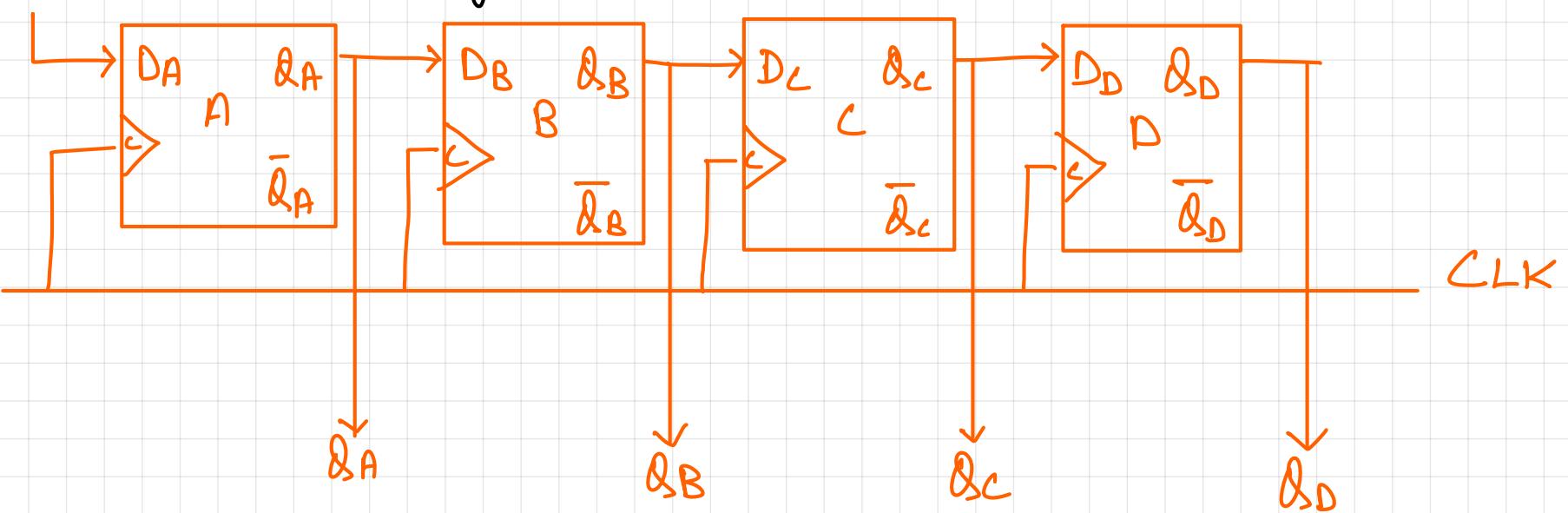


PIPO Register :-

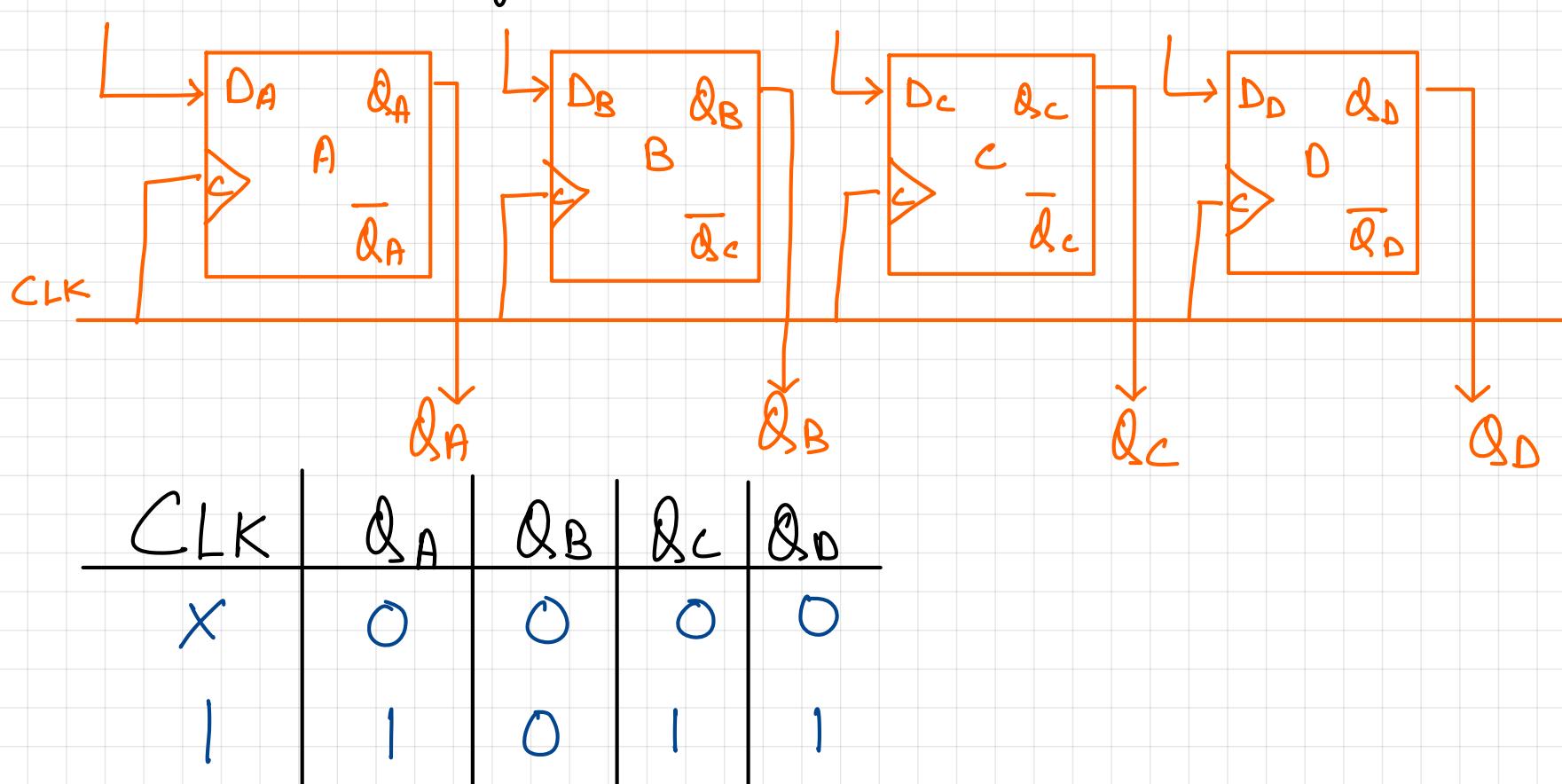


CLK	Q_A	Q_B	Q_C	Q_D
X	0	0	0	0
1	1	0	1	1

SISO / SIPO

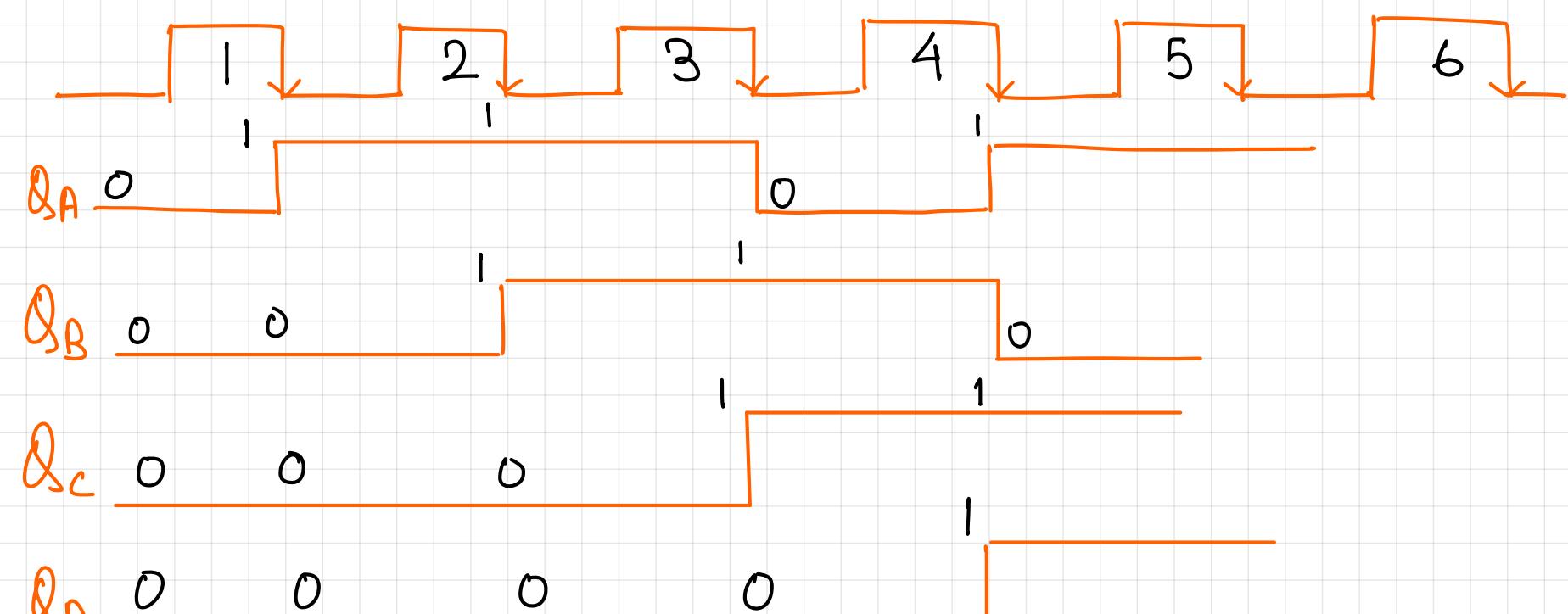


{ SISO \rightarrow for storing & SIPO \rightarrow for storing and getting output }

PIPO :-

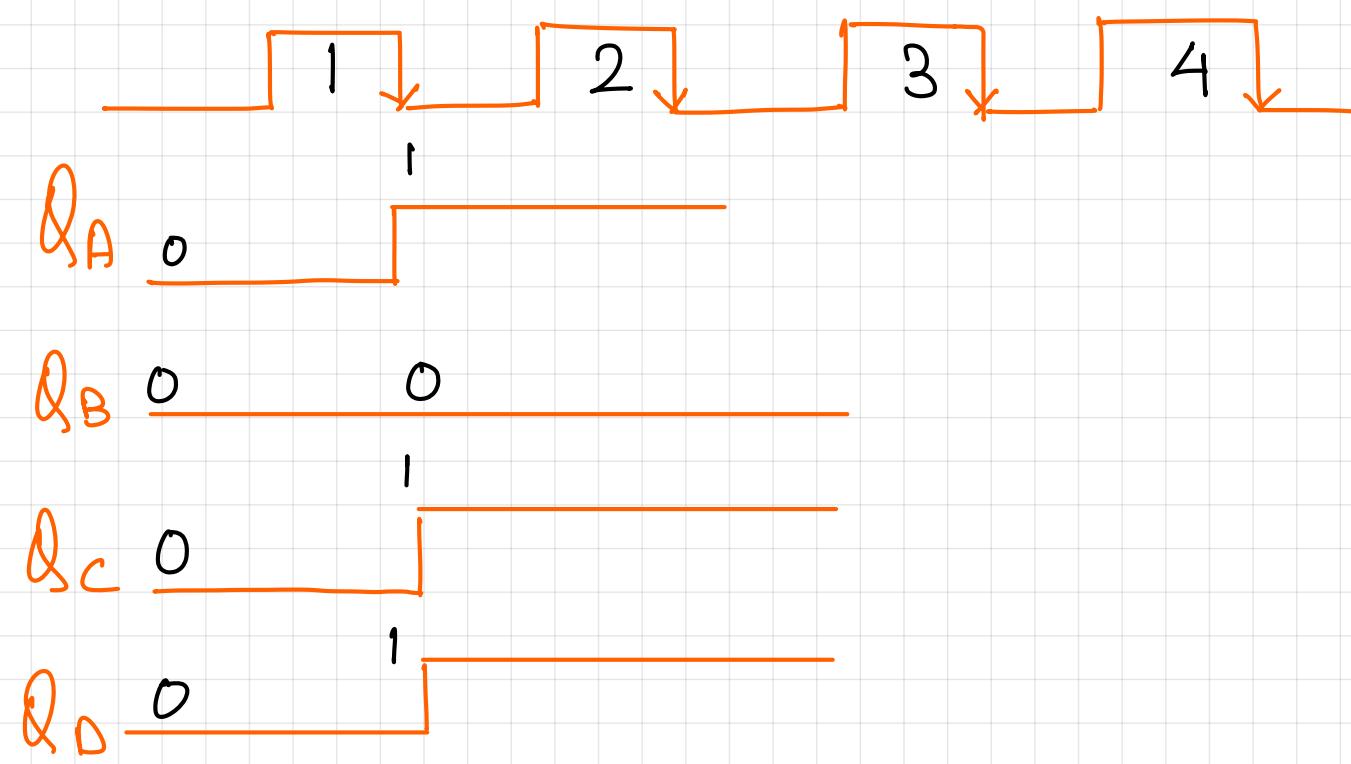


From SIPO (1010) :-

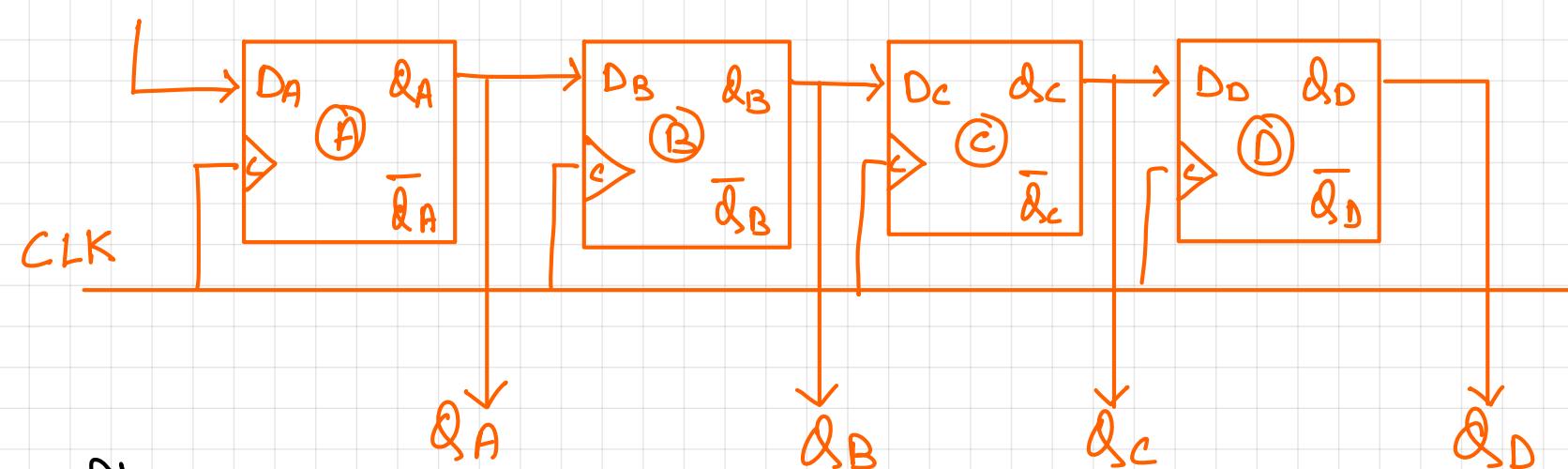


Truth Table :-

CLK	Q _A	Q _B	Q _C	Q _D
X	0	0	0	0
1	0	0	0	0
2	1	0	0	0
3	0	1	0	0
4	1	0	1	0


Waveform :-

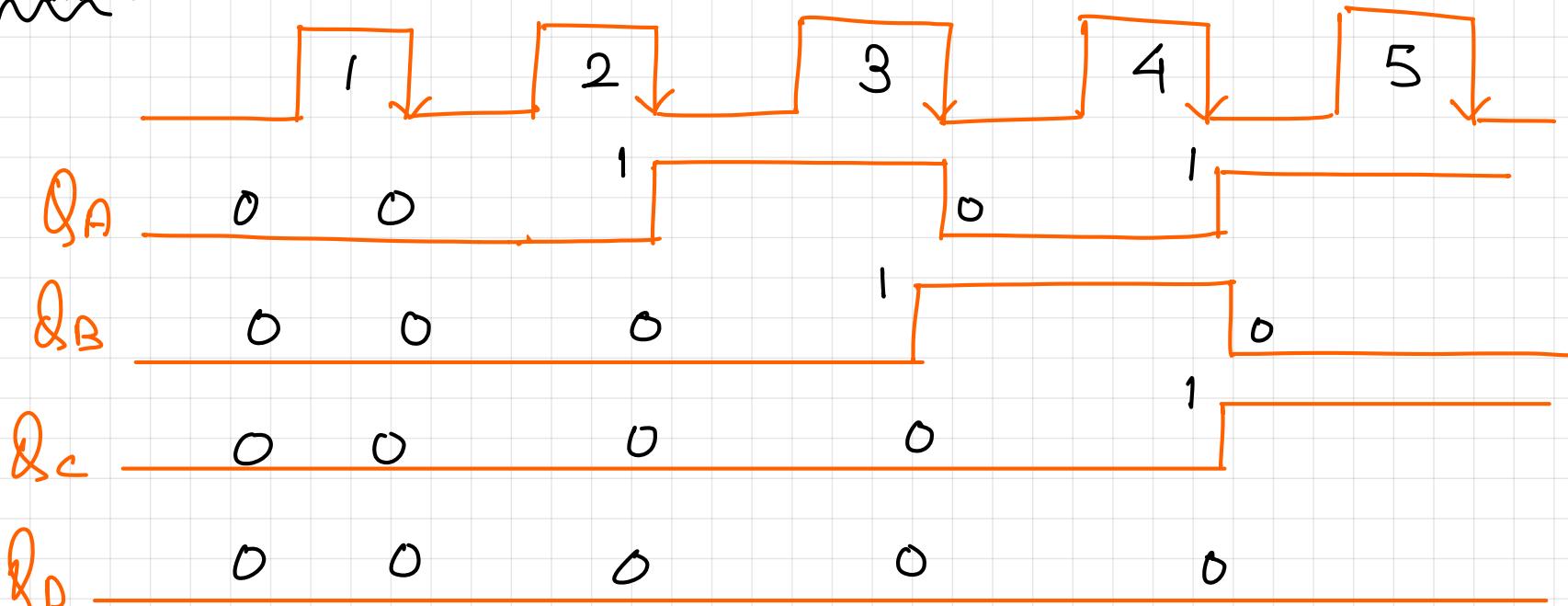

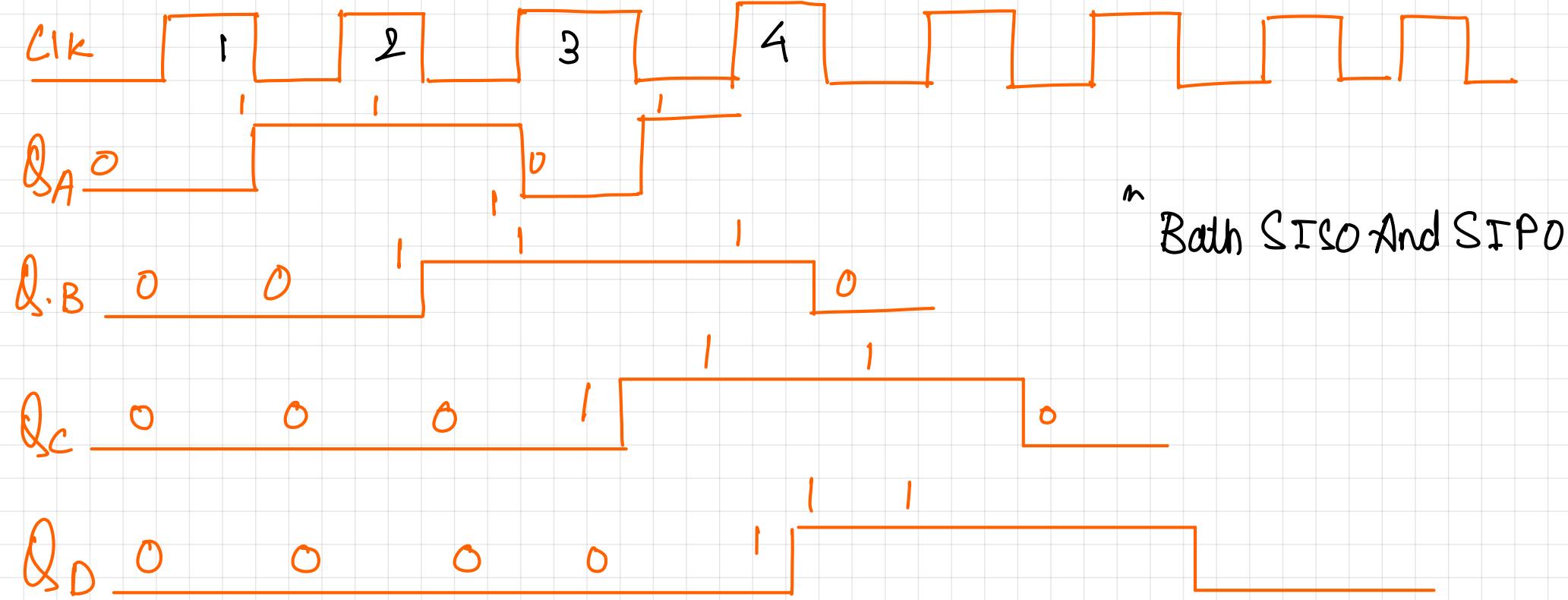

"Batch SISO And SIPO"

- For PIPD \rightarrow 1010.

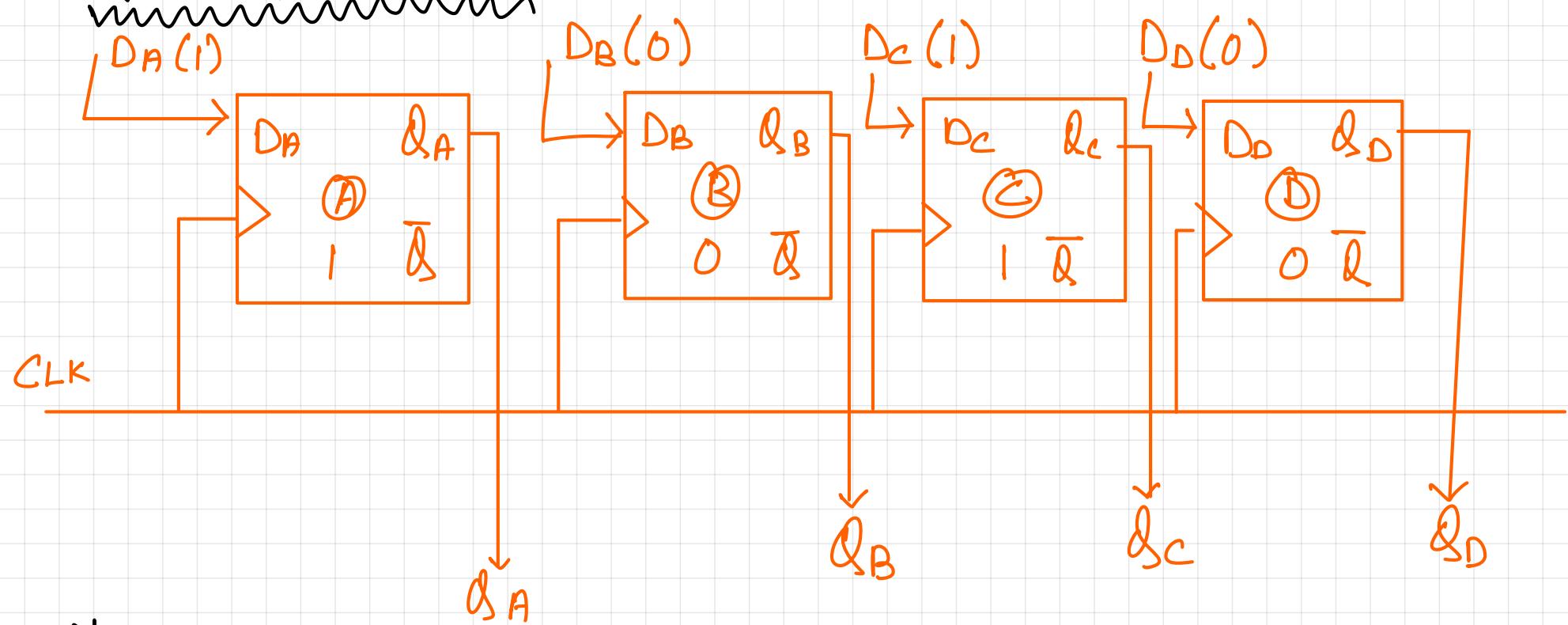

- Truth Table :-

CLK	Q_A	Q_B	Q_C	Q_D
X	0	0	0	0
1	1	0	1	0

- Waveform :-

